


COMP3222/9222 Digital Circuits & Systems

8. Digital System Design

Objectives


- Apply design techniques to comprehensive digital design problems
 - Consider the datapath components needed, the finite state machines required for their control and their description in VHDL
- Learn how digital systems comprising datapaths and control circuits can be derived from an ASM chart
- Look at a number of practical issues to do with real system inputs and outputs

Digital system

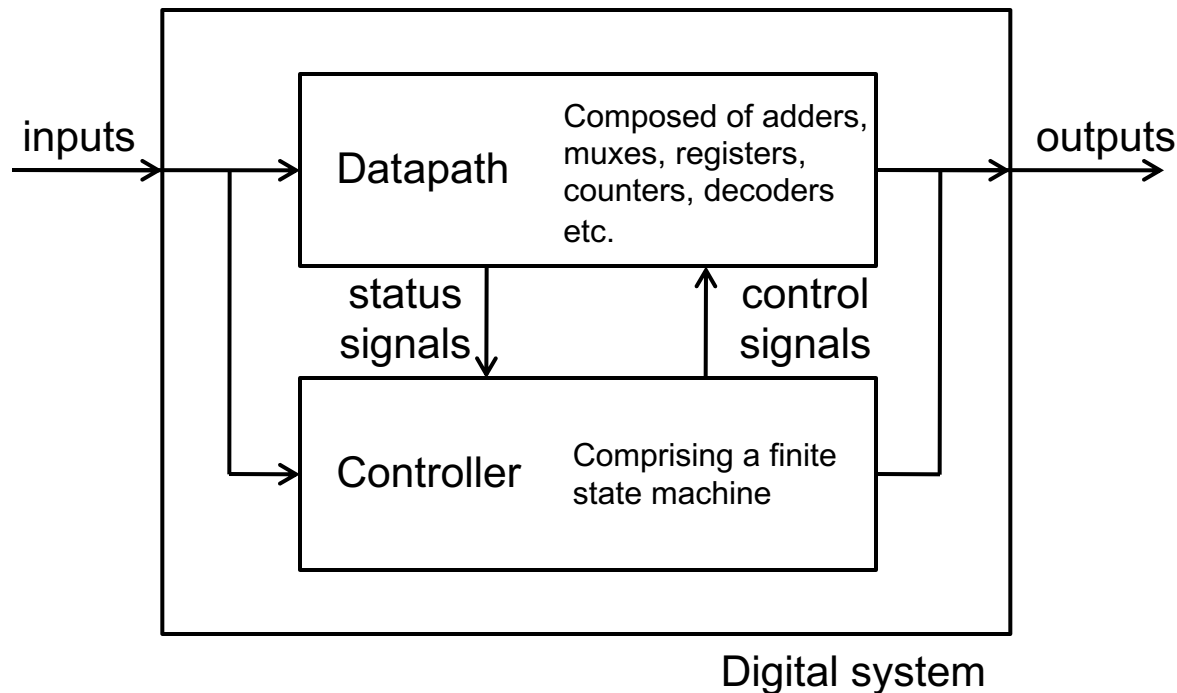


- A digital system comprises a *datapath*, which transforms the data as required by a specification, and a *controller* (control unit, control path), which supervises the operation of the datapath by monitoring its *status* and setting *control* signals
- The behaviour of both parts is conveniently modelled in an integrated manner using an Algorithmic State Machine (ASM) chart (see later)

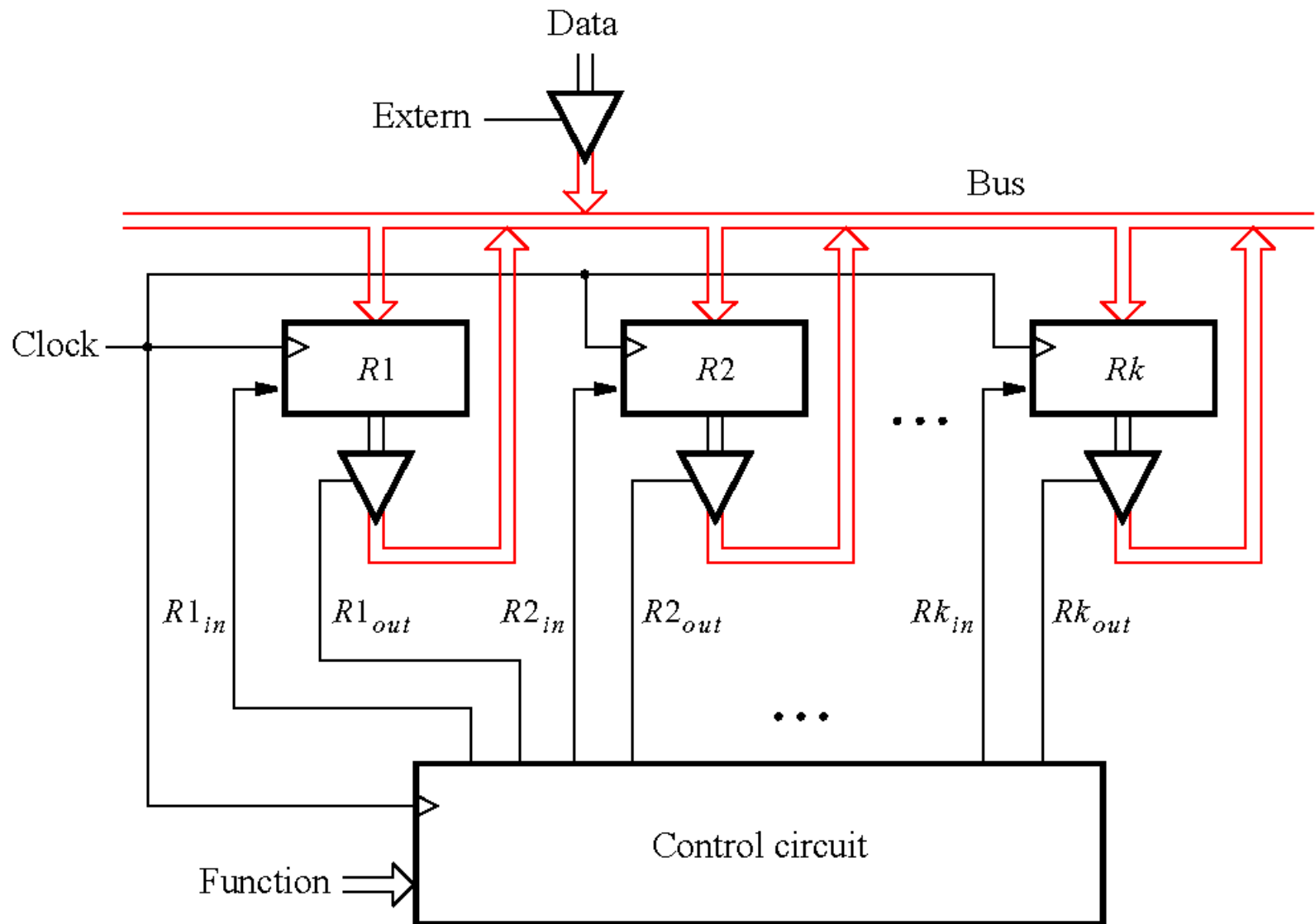Design Example 1 (pp 438-450): A digital system with k registers



Recall details for connecting registers to a bus

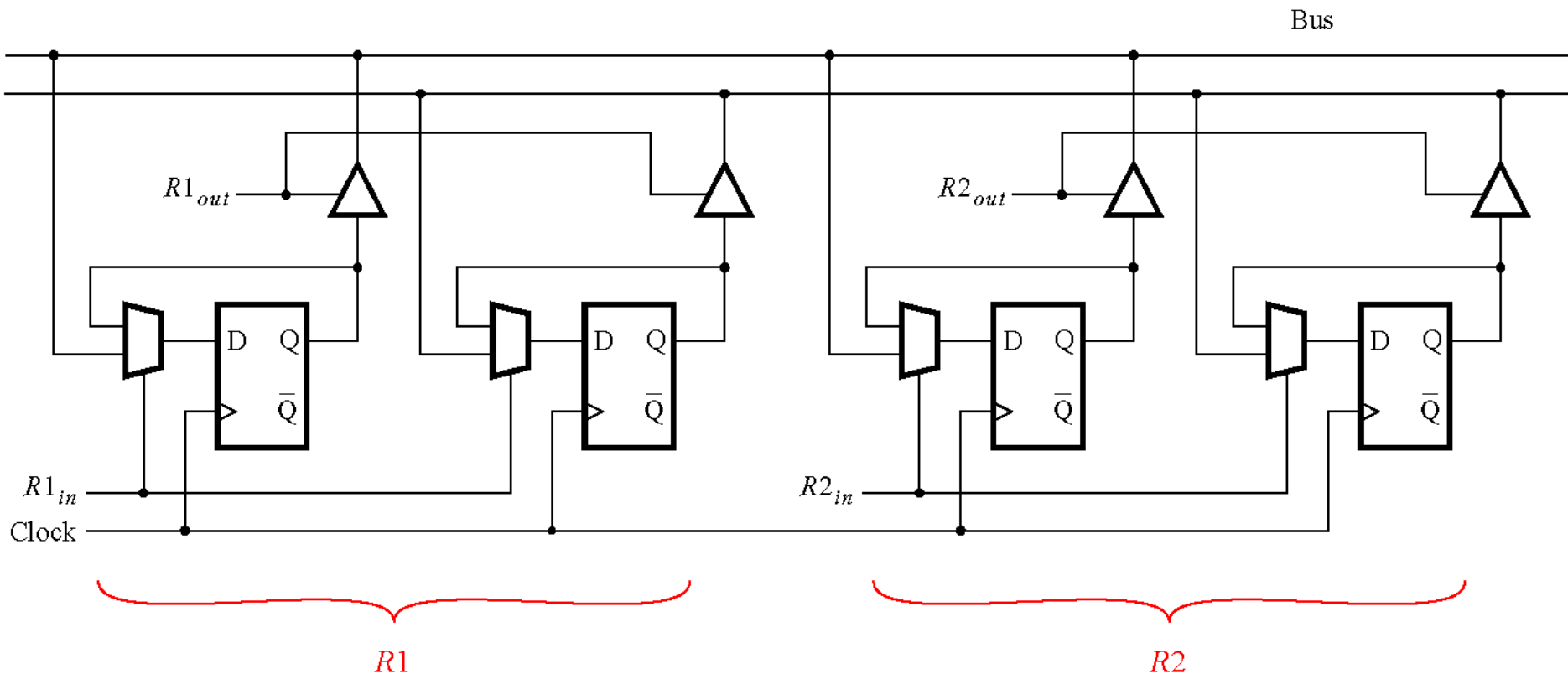- Consider two 2-bit registers
 - 3-state (tri-state) buffers used to avoid “tying” outputs together




Control circuit design

- Consider the control required to swap the contents of R1 and R2 using R3 for temporary storage
 - What are the individual *register transfers* required to effect the swap?
 - Which control signals need to be asserted for each transfer?
 - When & how should the control signals be sequenced?


In successive steps:

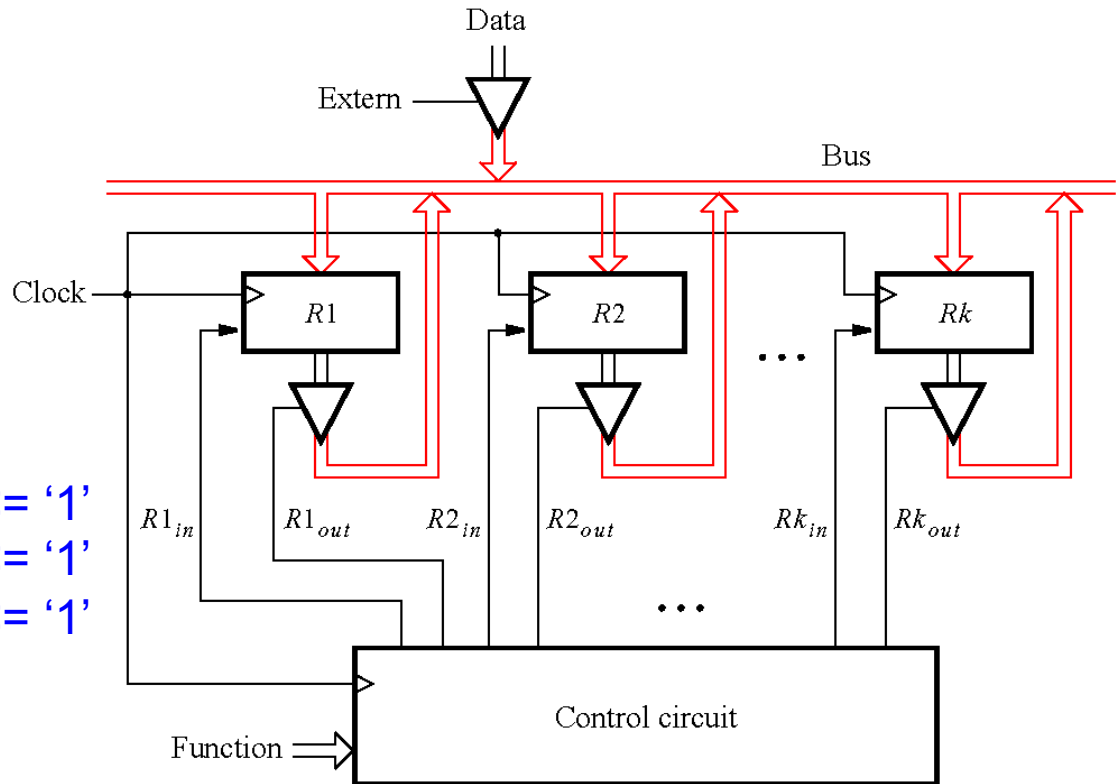1. $R3 \leftarrow R2$: $R3_{in} \leftarrow '1'$; $R2_{out} \leftarrow '1'$
2. $R2 \leftarrow R1$: $R2_{in} \leftarrow '1'$; $R1_{out} \leftarrow '1'$
3. $R1 \leftarrow R3$: $R1_{in} \leftarrow '1'$; $R3_{out} \leftarrow '1'$



A shift-register based control circuit

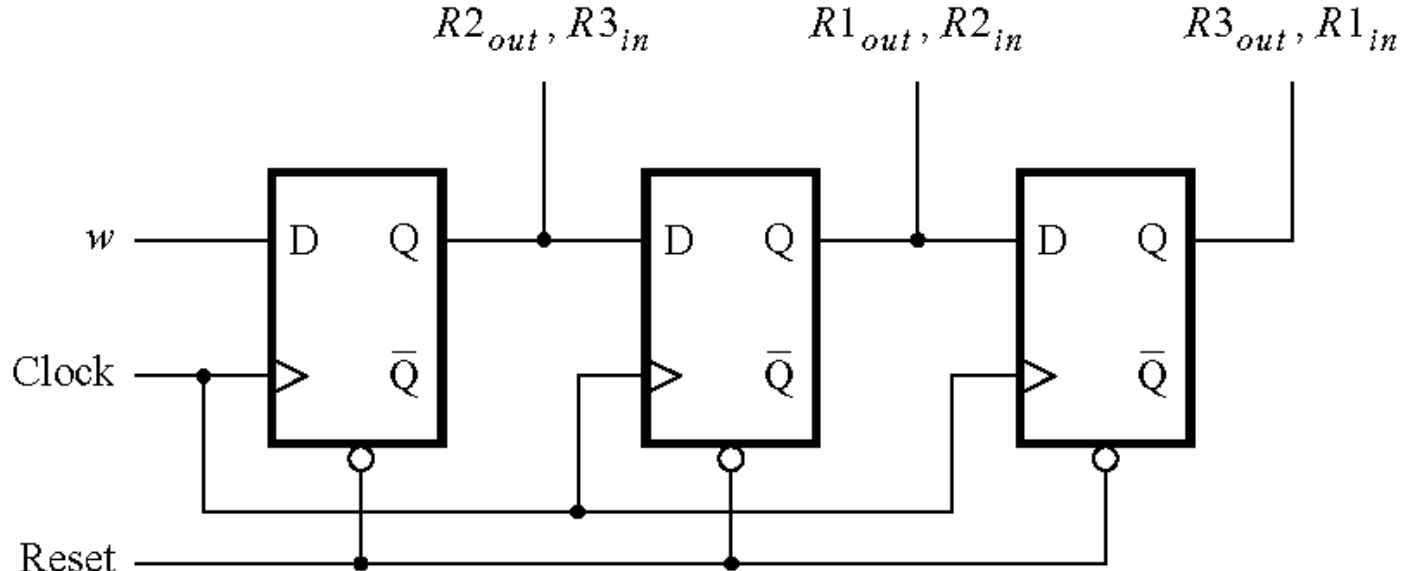- Swapping the contents of R1 and R2 using R3 for temporary storage
 - Could use *one-hot* control to enable 3-state buffers and loading of registers
 - Suffers delay of 1 cycle after input w asserted
 - Assumes w is deasserted for at least two clock cycles after the period



Code for an n -bit register with enable *Rin*

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY regne IS
    GENERIC ( N : INTEGER := 8 ) ;
    PORT ( R          : IN      STD_LOGIC_VECTOR(N-1 DOWNT0 0) ;
           Rin, Clock : IN      STD_LOGIC ;
           Q          : OUT     STD_LOGIC_VECTOR(N-1 DOWNT0 0) ) ;
END regne ;

ARCHITECTURE Behavior OF regne IS
BEGIN
    PROCESS
    BEGIN
        WAIT UNTIL Clock'EVENT AND Clock = '1' ;
        IF Rin = '1' THEN
            Q <= R ;
        END IF ;
    END PROCESS ;
END Behavior ;
```


Code for an *n*-bit 3-state buffer

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY trin IS
    GENERIC ( N : INTEGER := 8 ) ;
    PORT ( X   : IN      STD_LOGIC_VECTOR(N-1 DOWNT0 0) ;
          E   : IN      STD_LOGIC ;
          F   : OUT     STD_LOGIC_VECTOR(N-1 DOWNT0 0) ) ;
END trin ;

ARCHITECTURE Behavior OF trin IS
BEGIN
    F <= (OTHERS => 'Z') WHEN E = '0' ELSE X ;
END Behavior ;
```

Code for L-R shift register with reset

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY shiftr IS -- left-to-right shift register with async reset
    GENERIC ( K : INTEGER := 4 ) ;
    PORT ( Resetn, Clock, w : IN          STD_LOGIC ;
           Q : BUFFER STD_LOGIC_VECTOR(1 TO K) ) ;
END shiftr ;

ARCHITECTURE Behavior OF shiftr IS
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            Q <= (OTHERS => '0') ;
        ELSIF Clock'EVENT AND Clock = '1' THEN
            Genbits: FOR i IN K DOWNTO 2 LOOP
                Q(i) <= Q(i-1) ;
            END LOOP ;
            Q(1) <= w ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

Package and component declarations

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;
```

```
PACKAGE components IS
```

```
    COMPONENT regne -- register
```

```
        GENERIC ( N : INTEGER := 8 ) ;
```

```
        PORT ( R          : IN      STD_LOGIC_VECTOR(N-1 DOWNT0 0) ;
```

```
              Rin, Clock  : IN      STD_LOGIC ;
```

```
              Q           : OUT     STD_LOGIC_VECTOR(N-1 DOWNT0 0) ) ;
```

```
    END COMPONENT ;
```

```
    COMPONENT shiftr -- left-to-right shift register with async reset
```

```
        GENERIC ( K : INTEGER := 4 ) ;
```

```
        PORT ( Resetn, Clock, w : IN      STD_LOGIC ;
```

```
              Q                 : BUFFER  STD_LOGIC_VECTOR(1 TO K) ) ;
```

```
    END component ;
```

```
    COMPONENT trin -- 3-state buffers
```

```
        GENERIC ( N : INTEGER := 8 ) ;
```

```
        PORT ( X : IN      STD_LOGIC_VECTOR(N-1 DOWNT0 0) ;
```

```
              E : IN      STD_LOGIC ;
```

```
              F : OUT     STD_LOGIC_VECTOR(N-1 DOWNT0 0) ) ;
```

```
    END COMPONENT ;
```

```
END components ;
```

The digital system from L08/S6 used to swap R1 and R2 via R3

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE work.components.all ;
```

ENTITY swap IS

```
PORT ( Data      : IN      STD_LOGIC_VECTOR(7 DOWNTO 0) ;
      Resetn, w   : IN      STD_LOGIC ;
      Clock, Extern : IN      STD_LOGIC ;
      RinExt      : IN      STD_LOGIC_VECTOR(1 TO 3) ; -- allows regs to be externally loaded
      BusWires    : BUFFER  STD_LOGIC_VECTOR(7 DOWNTO 0) ;
```

END swap ;

ARCHITECTURE Structure OF swap IS


```
SIGNAL Rin, Rout, Q : STD_LOGIC_VECTOR(1 TO 3) ;
SIGNAL R1, R2, R3 : STD_LOGIC_VECTOR(7 DOWNTO 0) ;
```

BEGIN

```
control: shiftr GENERIC MAP ( K => 3 )
  PORT MAP ( Resetn, Clock, w, Q ) ;
Rin(1) <= RinExt(1) OR Q(3) ;
Rin(2) <= RinExt(2) OR Q(2) ;
Rin(3) <= RinExt(3) OR Q(1) ;
Rout(1) <= Q(2) ; Rout(2) <= Q(1) ; Rout(3) <= Q(3) ;
```


```
tri_ext: trin PORT MAP ( Data, Extern, BusWires ) ;
reg1: regn PORT MAP ( BusWires, Rin(1), Clock, R1 ) ;
reg2: regn PORT MAP ( BusWires, Rin(2), Clock, R2 ) ;
reg3: regn PORT MAP ( BusWires, Rin(3), Clock, R3 ) ;
tri1: trin PORT MAP ( R1, Rout(1), BusWires ) ;
tri2: trin PORT MAP ( R2, Rout(2), BusWires ) ;
tri3: trin PORT MAP ( R3, Rout(3), BusWires ) ;
```

END Structure ;

 


Controller

Datapath

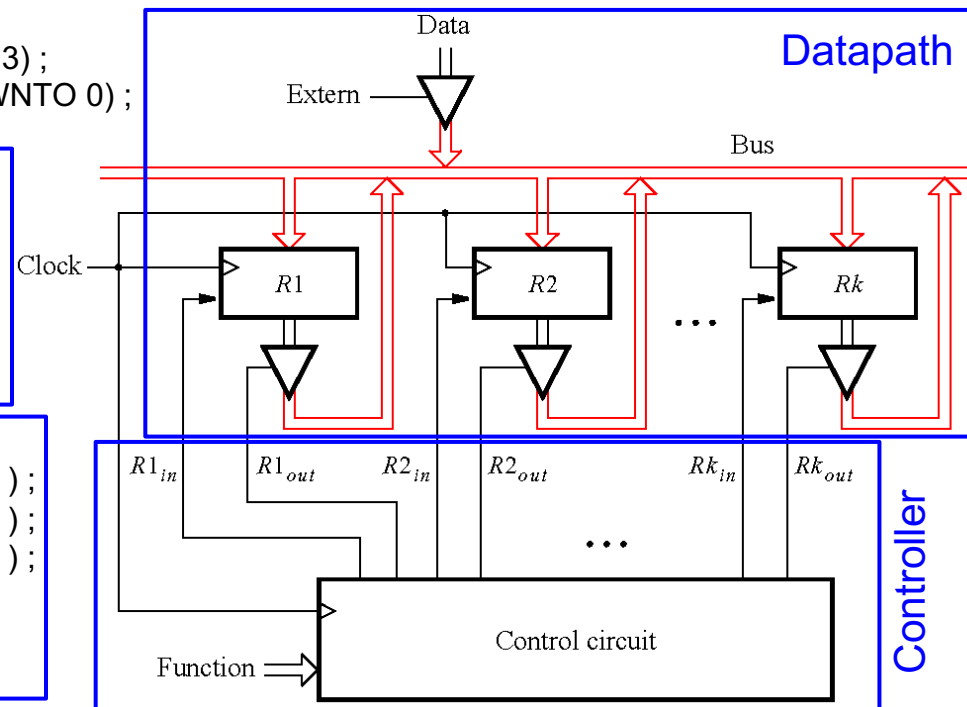

 
Timing simulation for the code of L08/S12



Code and waveform inputs to generate this waveform are available from the course website

Using multiplexers to implement a bus

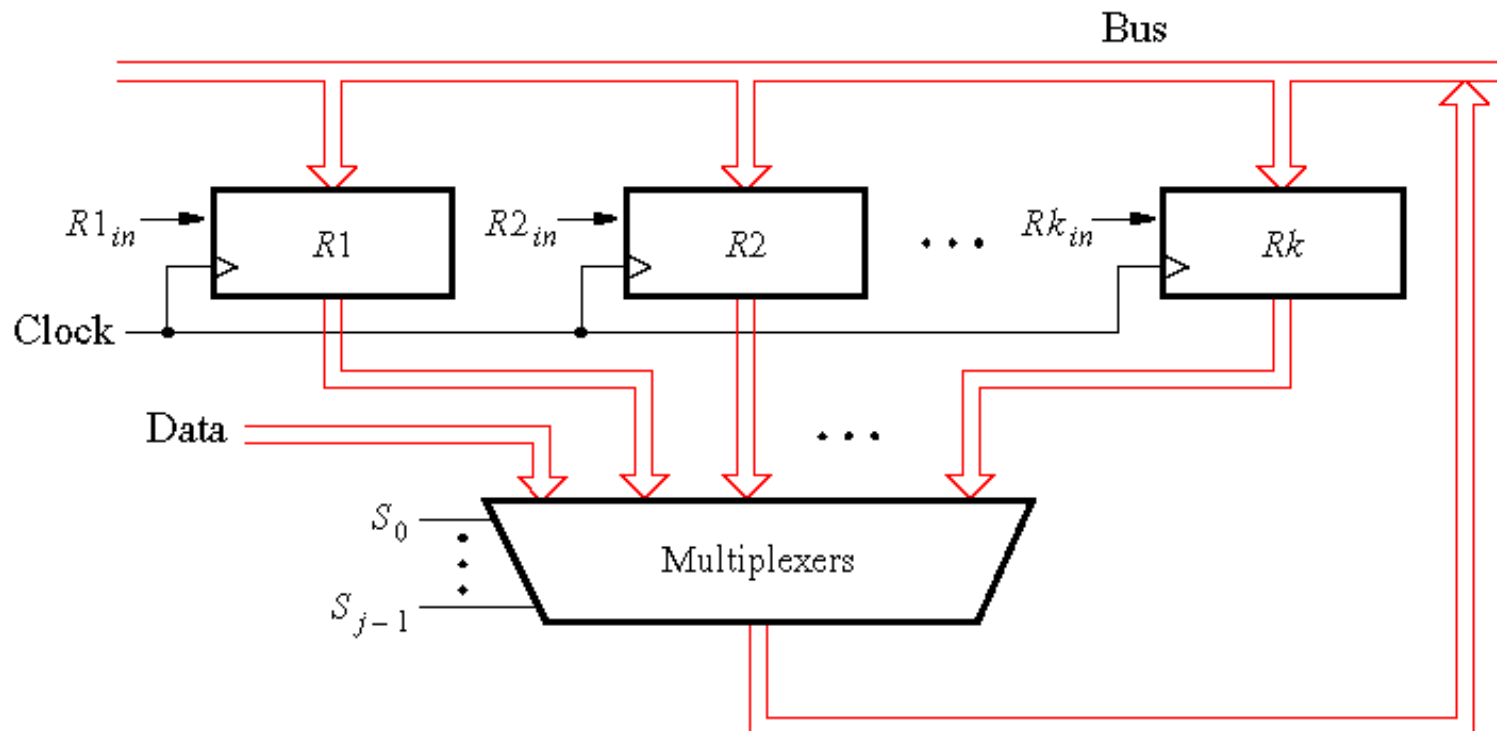- More typical to use MUXes instead of 3-state buffers since programmable devices (such as FPGAs) don't usually have many 3-state resources
- Both MUX and 3-state approaches are equally valid



Using multiplexers for swap

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE work.components.all ;
```

ENTITY swapmux IS

```
    PORT (Data      : IN      STD_LOGIC_VECTOR(7 DOWNTO 0) ;
          Resetn, w  : IN      STD_LOGIC ;
          Clock      : IN      STD_LOGIC ;
          RinExt      : IN      STD_LOGIC_VECTOR(1 TO 3) ;
          BusWires    : BUFFER  STD_LOGIC_VECTOR(7 DOWNTO 0) ) ;
```

END swapmux ;


ARCHITECTURE Mixed OF swapmux IS

```
    SIGNAL Rin, Q : STD_LOGIC_VECTOR(1 TO 3) ;
    SIGNAL R1, R2, R3 : STD_LOGIC_VECTOR(7 DOWNTO 0) ;
```


BEGIN

```
    control: shiftr GENERIC MAP ( K => 3 )
        PORT MAP ( Resetn, Clock, w, Q ) ;
    Rin(1) <= RinExt(1) OR Q(3) ;
    Rin(2) <= RinExt(2) OR Q(2) ;
    Rin(3) <= RinExt(3) OR Q(1) ;
    reg1: regn PORT MAP ( BusWires, Rin(1), Clock, R1 ) ;
    reg2: regn PORT MAP ( BusWires, Rin(2), Clock, R2 ) ;
    reg3: regn PORT MAP ( BusWires, Rin(3), Clock, R3 ) ;
    muxes: WITH Q SELECT
        BusWires <= Data WHEN "000",
                    R2 WHEN "100",
                    R1 WHEN "010",
                    R3 WHEN OTHERS ;
```

END Mixed ;

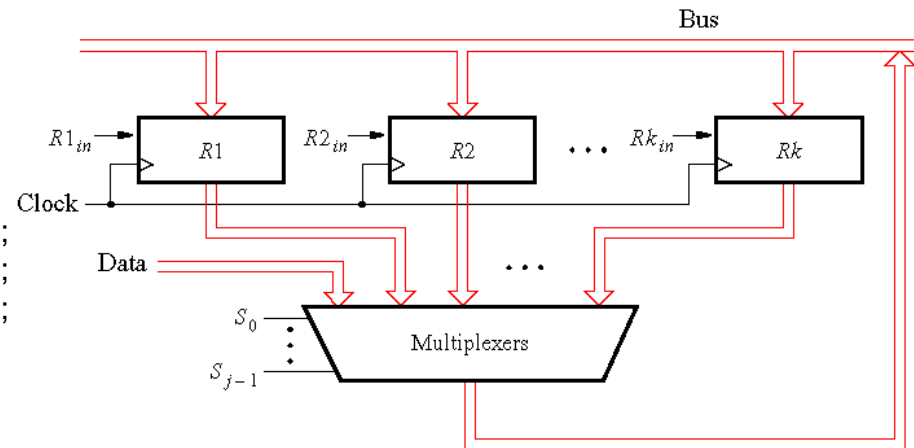


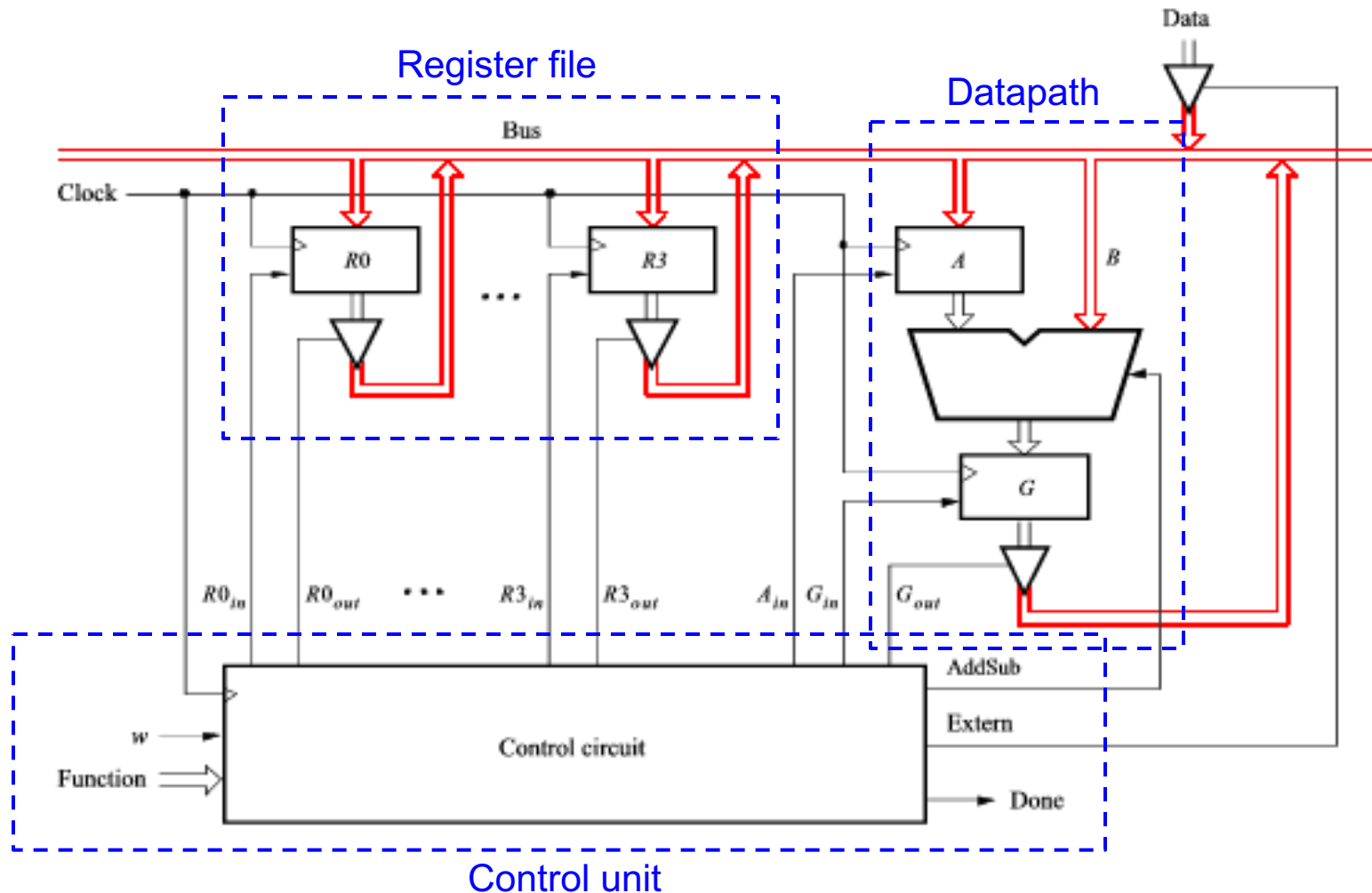Design Example 2 (pp 450-462): A simple processor




Operations performed by the processor

| Operation | Function performed |
|-----------------|-------------------------|
| Load $Rx, Data$ | $Rx \leftarrow Data$ |
| Move Rx, Ry | $Rx \leftarrow Ry$ |
| Add Rx, Ry | $Rx \leftarrow Rx + Ry$ |
| Sub Rx, Ry | $Rx \leftarrow Rx - Ry$ |

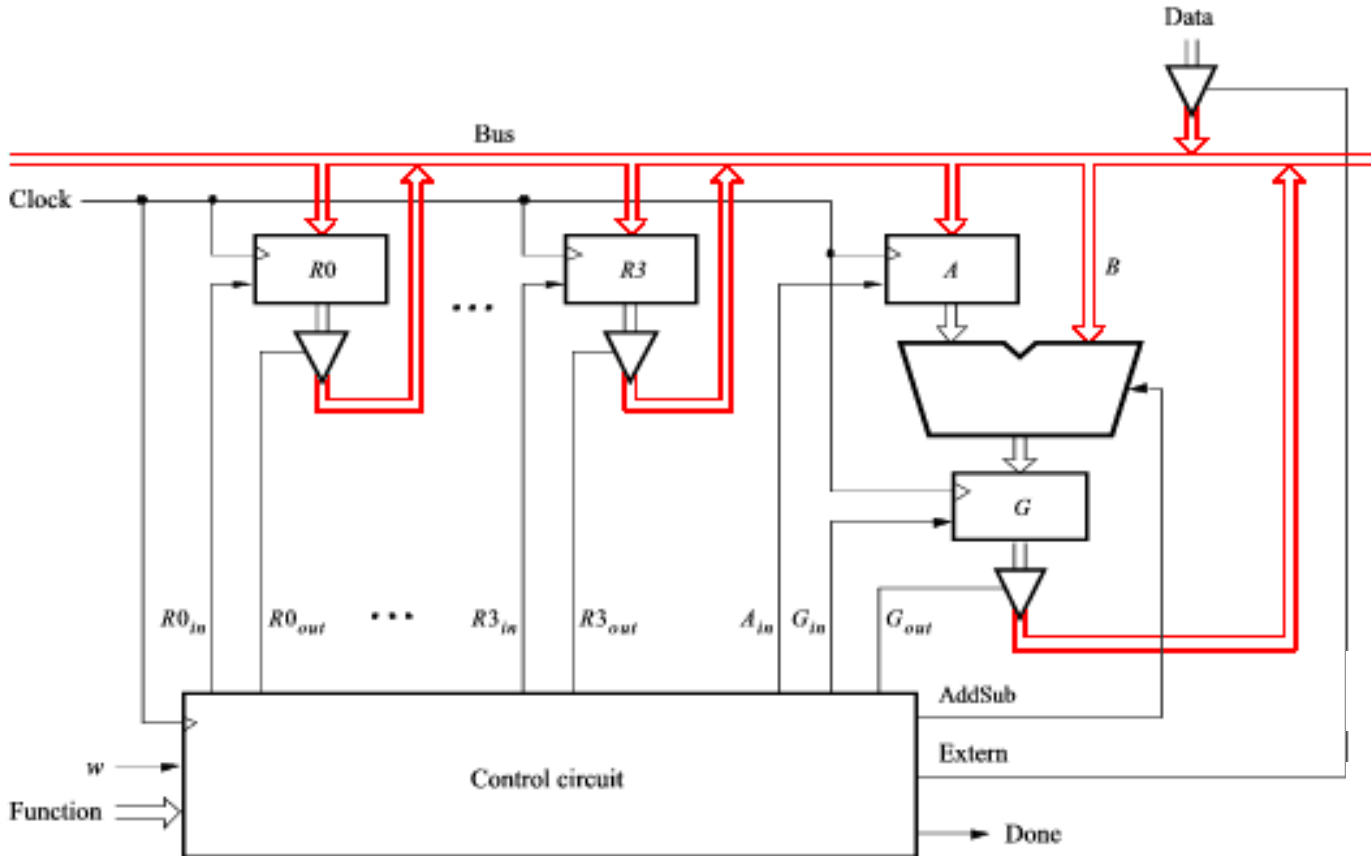

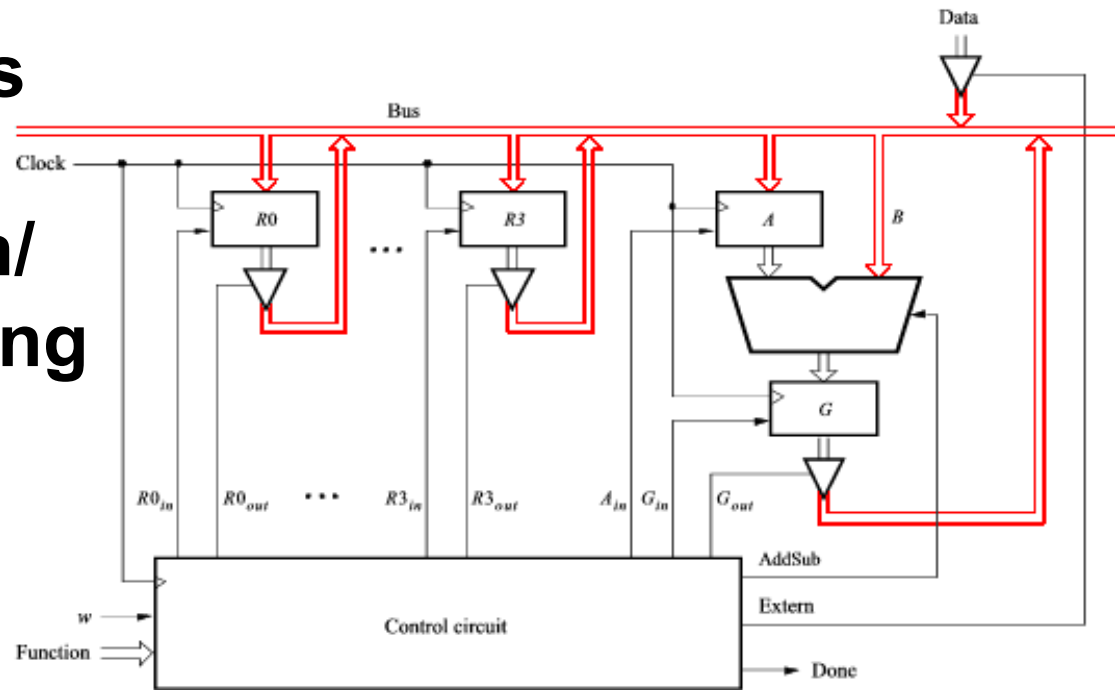
Control signals asserted in each operation/ time step (during each “micro-instruction”)




| | | <i>Control Signals</i> | | |
|-----------------------|------------------------------|------------------------|--------------------|--------------------|
| <i>Operation</i> | <i>Function</i> | <i>Time Step 1</i> | <i>Time Step 2</i> | <i>Time Step 3</i> |
| I_0 : Load Rx, Data | $R_x \leftarrow \text{Data}$ | | | |
| I_1 : Move Rx, Ry | $R_x \leftarrow R_y$ | | | |
| I_2 : Add Rx, Ry | $R_x \leftarrow R_x + R_y$ | | | |
| I_3 : Sub Rx, Ry | $R_x \leftarrow R_x - R_y$ | | | |

Keeping track of the instruction step

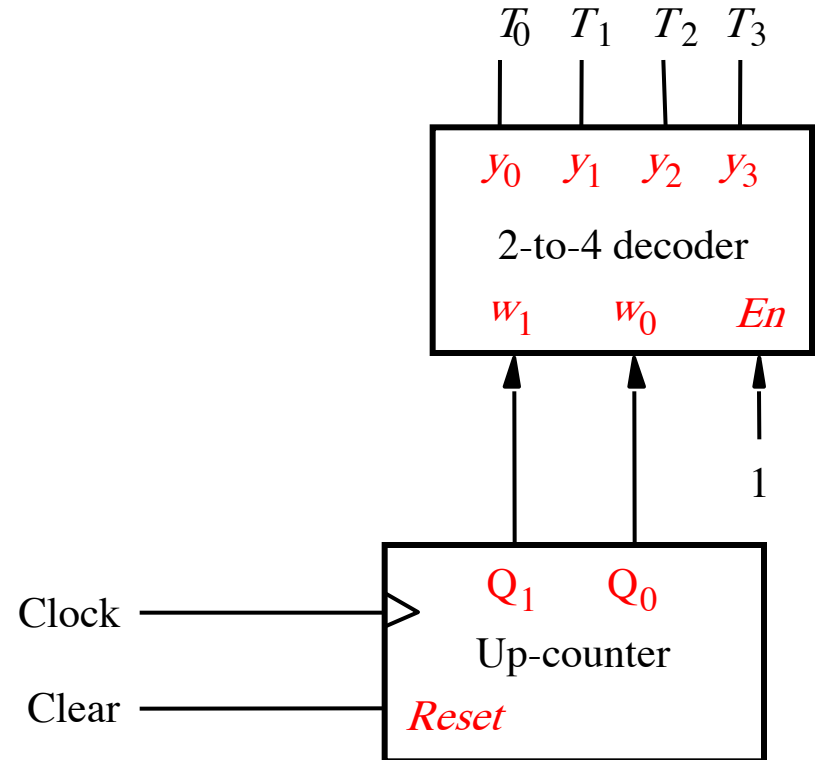- In Example 1 we used a shift register to keep track of which cycle we were in
- This time, let's use a counter, and decode it to obtain the instruction step
- $T_0 \Rightarrow$ not currently executing an instruction



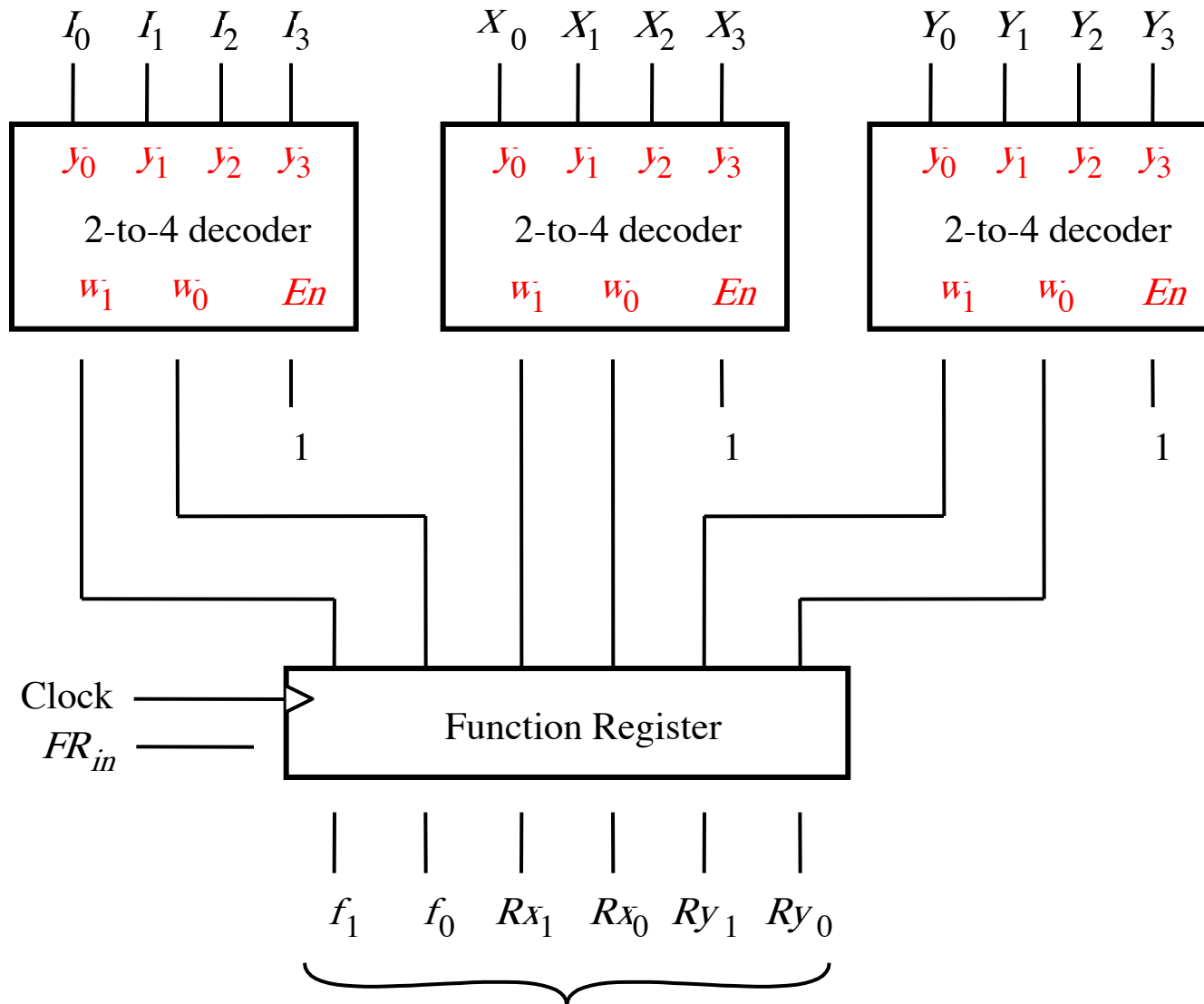In order to simplify derivation of control signals, save the function and decode its fields



Derivation of control equations (1)

- a) Clear instruction counter when *Reset* or *Done* or when in T_0 and w not asserted: $Clear = \bar{w}T_0 + Done + Reset$
- b) Load Function Register when w is asserted in T_0 : $FR_{in} = wT_0$
- c) All other control signals are derived from the table on slide L08/S18 depending upon the instruction being executed and the current time step e.g. *Extern* is only asserted in I_0 (*Load*) during T_1 i.e. $Extern = I_0T_1$
- d) *Done* is asserted at the end of T_1 for *Load* & *Move* and at the end of T_3 for *Add* & *Sub*: $Done = (I_0 + I_1)T_1 + (I_2 + I_3)T_3$

| | | Control Signals | | |
|-----------------------|-------------------------|--|--|--|
| Operation | Function | Time Step 1 | Time Step 2 | Time Step 3 |
| I_0 : Load Rx, Data | $Rx \leftarrow Data$ | <i>Extern</i> , $R_{in} = X$, <i>Done</i> | | |
| I_1 : Move Rx, Ry | $Rx \leftarrow Ry$ | $R_{in} = X$, $R_{out} = Y$, <i>Done</i> | | |
| I_2 : Add Rx, Ry | $Rx \leftarrow Rx + Ry$ | $R_{out} = X$, A_{in} | $R_{out} = Y$, G_{in} , <i>AddSub</i> = 0 | G_{out} , $R_{in} = X$, <i>Done</i> |
| I_3 : Sub Rx, Ry | $Rx \leftarrow Rx - Ry$ | $R_{out} = X$, A_{in} | $R_{out} = Y$, G_{in} , <i>AddSub</i> = 1 | G_{out} , $R_{in} = X$, <i>Done</i> |

Derivation of control equations (2)

e) $A_{in} = (I_2 + I_3)T_1$
 $G_{in} = (I_2 + I_3)T_2$
 $G_{out} = (I_2 + I_3)T_3$
 $AddSub = I_3$

| | | Control Signals | | |
|-----------------------|-----------------------------|--|--|------------------------------------|
| Operation | Function | Time Step 1 | Time Step 2 | Time Step 3 |
| I_0 : Load Rx, Data | $Rx \leftarrow \text{Data}$ | Extern, $R_{in} = X$, Done | | |
| I_1 : Move Rx, Ry | $Rx \leftarrow Ry$ | $R_{in} = X$, $R_{out} = Y$, Done | | |
| I_2 : Add Rx, Ry | $Rx \leftarrow Rx + Ry$ | $R_{out} = X$, A_{in} | $R_{out} = Y$, G_{in} , $AddSub = 0$ | G_{out} , $R_{in} = X$, Done |
| I_3 : Sub Rx, Ry | $Rx \leftarrow Rx - Ry$ | $R_{out} = X$, A_{in} | $R_{out} = Y$, G_{in} , $AddSub = 1$ | G_{out} , $R_{in} = X$, Done |

f) $R_0..R_3$ are determined from $X_0..X_3$ or $Y_0..Y_3$.

In the table from L08/S18, $R_{in} = X$ means the register corresponding to the asserted X value should be loaded. Thus we can derive

$$R0_{in} = (I_0 + I_1)T_1X_0 + (I_2 + I_3)T_3X_0 \quad \text{and}$$

$$R0_{out} = I_1T_1Y_0 + (I_2 + I_3)(T_1X_0 + T_2Y_0)$$

Similar expressions can be derived for $R1_{in}..R3_{in}$ and $R1_{out}..R3_{out}$.

Code for a two-bit up-counter with synchronous reset

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;

ENTITY upcount IS
    PORT ( Clear, Clock : IN          STD_LOGIC ;
          Q              : BUFFER    STD_LOGIC_VECTOR(1 DOWNTO 0) ) ;
END upcount ;

ARCHITECTURE Behavior OF upcount IS
BEGIN
    upcount: PROCESS ( Clock )
    BEGIN
        IF (Clock'EVENT AND Clock = '1') THEN
            IF Clear = '1' THEN
                Q <= "00" ;
            ELSE
                Q <= Q + '1' ;
            END IF ;
        END IF ;
    END PROCESS;
END Behavior ;
```

Code for the processor (Part a)

- This code is for a 3-state, bus-based processor

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_signed.all ;
USE work.subccts.all ;

ENTITY proc IS
    PORT ( Data: IN STD_LOGIC_VECTOR(7 DOWNT0 0) ;
          Reset, w : IN STD_LOGIC ;
          Clock: IN STD_LOGIC ;
          F, Rx, Ry: IN STD_LOGIC_VECTOR(1 DOWNT0 0) ;
          Done: BUFFER STD_LOGIC ;
          BusWires: BUFFER STD_LOGIC_VECTOR(7 DOWNT0 0) ) ;
END proc ;

ARCHITECTURE Mixed OF proc IS
    SIGNAL Rin, Rout : STD_LOGIC_VECTOR(0 TO 3) ;
    SIGNAL Clear, High, AddSub : STD_LOGIC ;
    SIGNAL Extern, Ain, Gin, Gout, FRin : STD_LOGIC ;
    SIGNAL Count : STD_LOGIC_VECTOR(1 DOWNT0 0) ;
    SIGNAL T, I, X, Y : STD_LOGIC_VECTOR(0 TO 3) ;
    SIGNAL R0, R1, R2, R3 : STD_LOGIC_VECTOR(7 DOWNT0 0) ;
    SIGNAL A, Sum, G : STD_LOGIC_VECTOR(7 DOWNT0 0) ;
    SIGNAL Func, FuncReg : STD_LOGIC_VECTOR(1 TO 6) ;
```

```
BEGIN
    High <= '1' ;
    Clear <= Reset OR Done OR (NOT w AND T(0)) ;
    counter: upcount PORT MAP ( Clear, Clock, Count ) ;
    decT: dec2to4 PORT MAP ( Count, High, T ) ;
    Func <= F & Rx & Ry ;
    FRin <= w AND T(0) ;
    functionreg: regn GENERIC MAP ( N => 6 )
        PORT MAP ( Func, FRin, Clock, FuncReg ) ;
    decl: dec2to4 PORT MAP ( FuncReg(1 TO 2), High, I ) ;
    decX: dec2to4 PORT MAP ( FuncReg(3 TO 4), High, X ) ;
    decY: dec2to4 PORT MAP ( FuncReg(5 TO 6), High, Y ) ;

    Extern <= I(0) AND T(1) ;
    Done <= ((I(0) OR I(1)) AND T(1)) OR ((I(2) OR I(3)) AND T(3)) ;
    Ain <= (I(2) OR I(3)) AND T(1) ;
    Gin <= (I(2) OR I(3)) AND T(2) ;
    Gout <= (I(2) OR I(3)) AND T(3) ;
    AddSub <= I(3) ;

    ... continued in Part b.
```

Controller (continued on next page)

Code for the processor (Part *b*)

RegCntl:

Controller

FOR k IN 0 TO 3 GENERATE

Rin(k) <= ((I(0) OR I(1)) AND T(1) AND X(k)) OR
((I(2) OR I(3)) AND T(3) AND X(k)) ;

Rout(k) <= (I(1) AND T(1) AND Y(k)) OR
((I(2) OR I(3)) AND ((T(1) AND X(k)) OR (T(2) AND Y(k)))) ;

END GENERATE RegCntl ;

tri_extrn: trin PORT MAP (Data, Extern, BusWires) ;

reg0: regn PORT MAP (BusWires, Rin(0), Clock, R0) ;

reg1: regn PORT MAP (BusWires, Rin(1), Clock, R1) ;

reg2: regn PORT MAP (BusWires, Rin(2), Clock, R2) ;

reg3: regn PORT MAP (BusWires, Rin(3), Clock, R3) ;

tri0: trin PORT MAP (R0, Rout(0), BusWires) ;

tri1: trin PORT MAP (R1, Rout(1), BusWires) ;

tri2: trin PORT MAP (R2, Rout(2), BusWires) ;

tri3: trin PORT MAP (R3, Rout(3), BusWires) ;

regA: regn PORT MAP (BusWires, Ain, Clock, A) ;

alu:

WITH AddSub SELECT

Sum <= A + BusWires WHEN '0',
A - BusWires WHEN OTHERS ;

regG: regn PORT MAP (Sum, Gin, Clock, G) ;

triG: trin PORT MAP (G, Gout, BusWires) ;

Datapath

END Mixed ;

Alternative code for a MUX-based processor

(Part a)

- Uses the same entity description as before
- Note that the table from slide L08/S18 is implemented directly

T, I not decoded to simplify CASE selection in controlsignals PROCESS

ALL outputs cleared by default at start of PROCESS to avoid risk of implying memory

```

ARCHITECTURE Mixed OF proc IS
    SIGNAL X, Y, Rin, Rout : STD_LOGIC_VECTOR(0 TO 3);
    SIGNAL Clear, High, AddSub : STD_LOGIC;
    SIGNAL Extern, Ain, Gin, Gout, FRin : STD_LOGIC;
    SIGNAL Count, T, I : STD_LOGIC_VECTOR(1 DOWNT0 0);
    SIGNAL R0, R1, R2, R3 : STD_LOGIC_VECTOR(7 DOWNT0 0);
    SIGNAL A, Sum, G : STD_LOGIC_VECTOR(7 DOWNT0 0);
    SIGNAL Func, FuncReg, Sel : STD_LOGIC_VECTOR(1 TO 6);
BEGIN
    High <= '1';
    Clear <= Reset OR Done
        OR (NOT w AND NOT T(1) AND NOT T(0));
    counter: upcount PORT MAP ( Clear, Clock, Count );
    T <= Count;
    Func <= F & Rx & Ry;
    FRin <= w AND NOT T(1) AND NOT T(0);
    functionreg: regn GENERIC MAP ( N => 6 )
        PORT MAP ( Func, FRin, Clock, FuncReg );
    I <= FuncReg(1 TO 2);
    decX: dec2to4 PORT MAP ( FuncReg(3 TO 4), High, X );
    decY: dec2to4 PORT MAP ( FuncReg(5 TO 6), High, Y );

    controlsignals: PROCESS ( T, I, X, Y )
    BEGIN
        Extern <= '0'; Done <= '0'; Ain <= '0'; Gin <= '0';
        Gout <= '0'; AddSub <= '0'; Rin <= "0000"; Rout <= "0000";
        CASE T IS WHEN "00" => -- no signals asserted in time step T0
        WHEN "01" => -- define signals asserted in time step T1
            CASE I IS
                WHEN "00" => -- Load
                    Extern <= '1'; Rin <= X; Done <= '1';
                WHEN "01" => -- Move
                    Rout <= Y; Rin <= X; Done <= '1';
                WHEN OTHERS => -- Add, Sub
                    Rout <= X; Ain <= '1';
            END CASE;
        END CASE;
    END PROCESS;
    ... continued in Part b

```

Controller

Alternative code for a MUX-based processor (Part *b*)

```
WHEN "10" => -- define signals asserted in time step T2
CASE I IS
    WHEN "10" => -- Add
        Rout <= Y ; Gin <= '1' ;
    WHEN "11" => -- Sub
        Rout <= Y ; AddSub <= '1' ; Gin <= '1' ;
    WHEN OTHERS => -- Load, Move
END CASE ;
WHEN OTHERS => -- define signals asserted in time step T3
CASE I IS
    WHEN "00" => -- Load
    WHEN "01" => -- Move
    WHEN OTHERS => -- Add, Sub
        Gout <= '1' ; Rin <= X ; Done <= '1' ;
END CASE ;
END CASE ;
END PROCESS ;
```

Controller

```
reg0: regn PORT MAP ( BusWires, Rin(0), Clock, R0 ) ;
reg1: regn PORT MAP ( BusWires, Rin(1), Clock, R1 ) ;
reg2: regn PORT MAP ( BusWires, Rin(2), Clock, R2 ) ;
reg3: regn PORT MAP ( BusWires, Rin(3), Clock, R3 ) ;
regA: regn PORT MAP ( BusWires, Ain, Clock, A ) ;
alu: WITH AddSub SELECT
    Sum <= A + BusWires WHEN '0',
        A - BusWires WHEN OTHERS ;
regG: regn PORT MAP ( Sum, Gin, Clock, G ) ;
Sel <= Rout & Gout & Extern ;
WITH Sel SELECT
    BusWires <=
        R0 WHEN "100000",
        R1 WHEN "010000",
        R2 WHEN "001000",
        R3 WHEN "000100",
        G WHEN "000010",
        Data WHEN OTHERS ;
END Mixed ;
```

Datapath


END Mixed ;

- Both versions have equivalent functionality
- However, the behavioural style used to capture the control signalling in the second version is less prone to error in deriving and coding the control equations

Functional simulation of the MUX-based processor

- Code and waveform inputs to generate this waveform are available from the course website

Stimuli (external signals)

 


Response
(internal signals)

load R0, #2A

Functional simulation of the MUX-based processor

- Code and waveform inputs to generate this waveform are available from the course website

Stimuli (external signals)

 


Response
(internal signals)

load R1, #55

Functional simulation of the MUX-based processor

- Code and waveform inputs to generate this waveform are available from the course website

Stimuli (external signals)

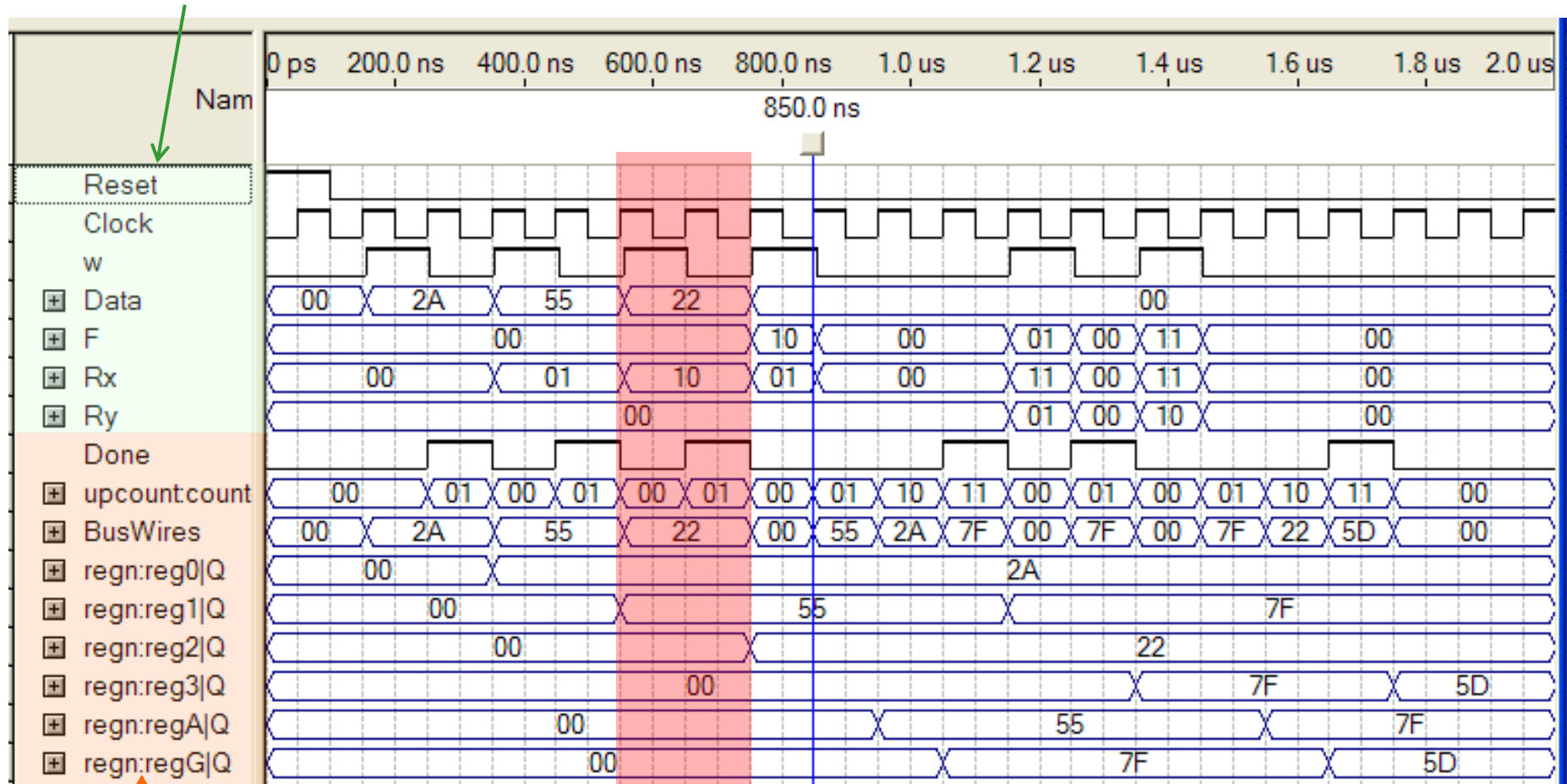


Response
(internal signals)

load R2, #22

Functional simulation of the MUX-based processor

- Code and waveform inputs to generate this waveform are available from the course website


Stimuli (external signals)

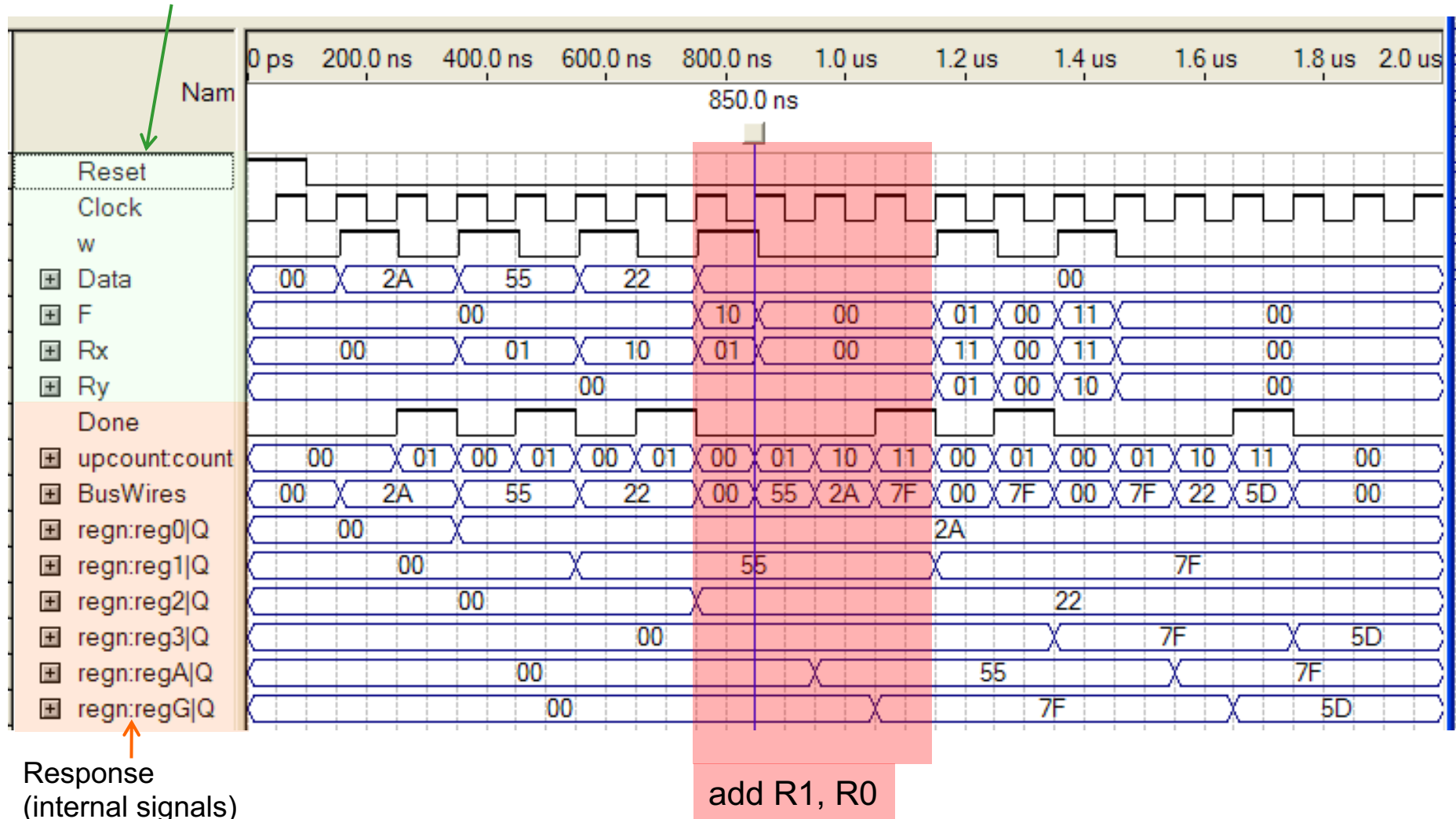

Functional simulation of the MUX-based processor

- Code and waveform inputs to generate this waveform are available from the course website


Stimuli (external signals)

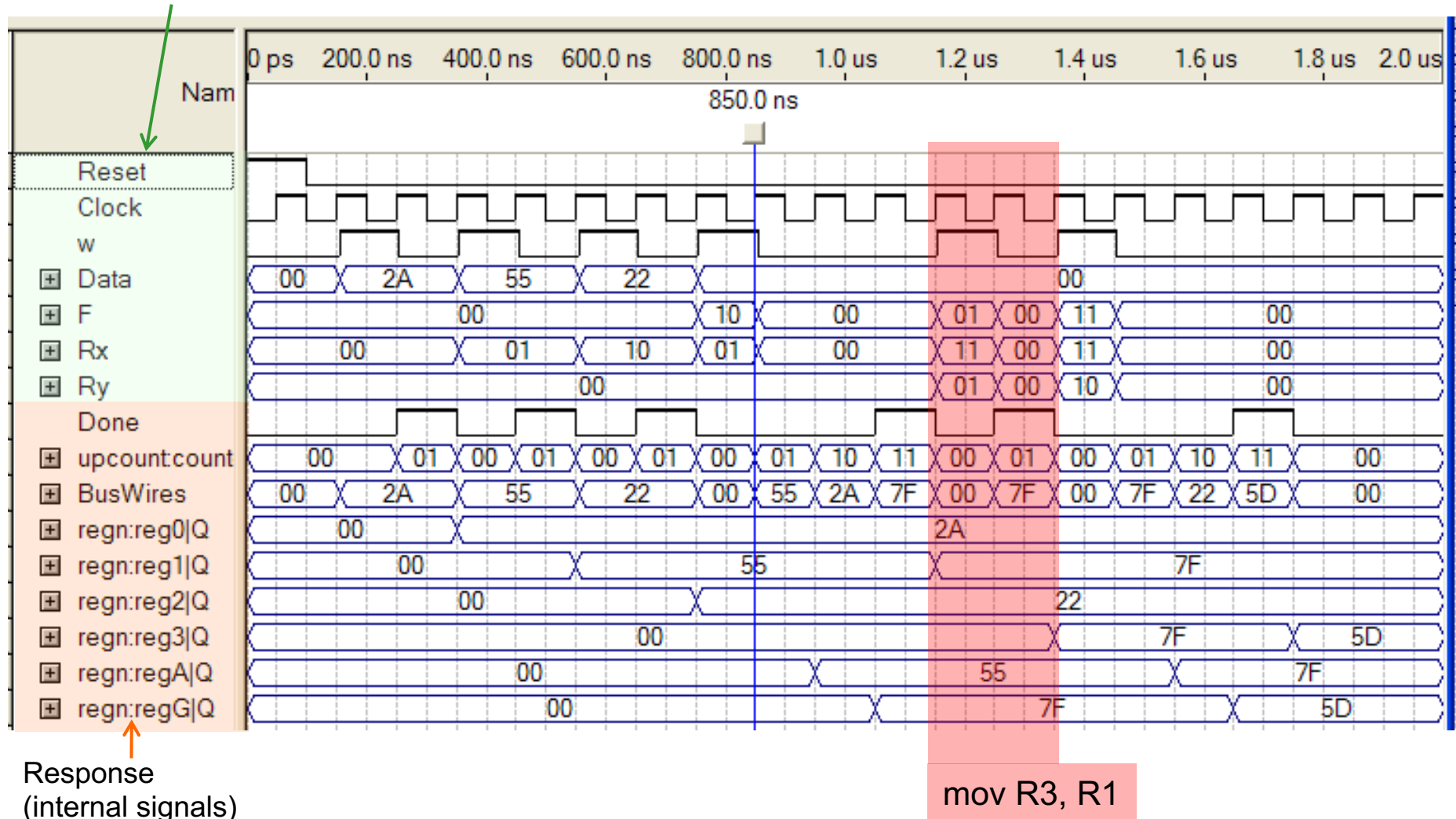

Functional simulation of the MUX-based processor

- Code and waveform inputs to generate this waveform are available from the course website

Stimuli (external signals)

 

Response
(internal signals)

sub R3, R2

Mapping the processor to our board


```
library ieee;
use ieee.std_logic_1164.all;
use work.subccts.all;
use work.proc_pkg.all;

entity mapproc is
    port (sw: in std_logic_vector(9 downto 0);
          key: in std_logic_vector(2 downto 0);
          ledr: out std_logic_vector(9 downto 0); --DE1
          hex0: out std_logic_vector(0 to 6);
          hex1: out std_logic_vector(0 to 6);
          hex2: out std_logic_vector(0 to 6);
          hex3: out std_logic_vector(0 to 6));
end mapproc;

architecture structural of mapproc is
    signal done, reset, w, clock: std_logic;
    signal buswires: std_logic_vector(3 downto 0);
    signal r0,r1,r2,r3: std_logic_vector(3 downto 0);
```

```
begin
    clock <= not key(0);
    reset <= not key(1);
    w <= not key(2);
    ledr(9) <= done; --DE1
    ledr(3 downto 0) <= buswires; --DE1
    proc0: proc
        generic map (L => 4)
        port map(Data => sw(3 downto 0),
                 Reset => reset, w => w,
                 Clock => clock,
                 F => sw(9 downto 8),
                 RX => sw(7 downto 6),
                 RY => sw(5 downto 4),
                 Done => done, BusWires => buswires,
                 R0 => r0, R1 => r1, R2 => r2,
                 R3 => r3);
    dig0: seg7 PORT map ( r0, hex0);
    dig1: seg7 PORT map ( r1, hex1);
    dig2: seg7 PORT map ( r2, hex2);
    dig3: seg7 PORT map ( r3, hex3);
end structural;
```


Simulating the mapping

 


Algorithmic state machines

- Algorithmic state machines (ASMs) are a type of flowchart
 - They are used to represent more complex (larger) FSMs that are impractical to represent using state diagrams and state tables
 - They can be used to represent the state transitions and generated outputs for an FSM
- There are three types of elements in ASM charts


Elements used in ASM charts

 

(a) Named state box


 


(b) Decision box

 

(c) Conditional output box



ASM chart for the FSM of L06/S10

  

B&V3, Figure 8.87

L08/S38

ASM chart for the FSM of L06/S23

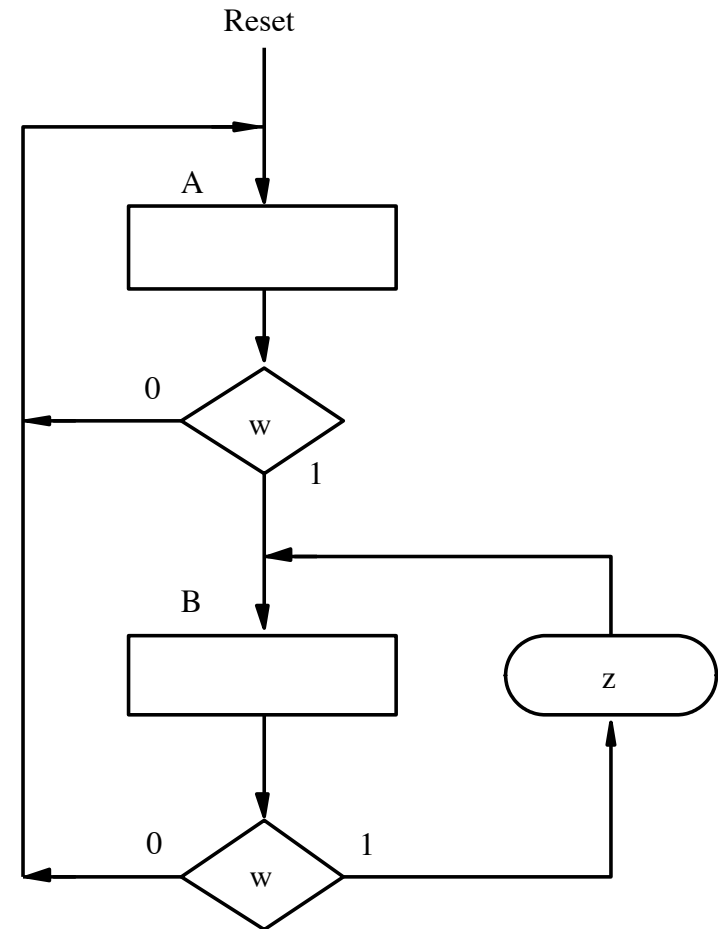 

Design Exercise 1:

pp 679 – 683, B&V3

- Devise a circuit that will count the number of ON bits in a data word

Pseudo-code for a bit counter (popcount)

input: A -- the word whose ON bits are to be counted


output: B -- the count of the number of ON bits in A

```
 $B = 0$   
while  $A \neq 0$  do  
  if  $a_0 = 1$  then  
     $B = B + 1$   
  end if  
  right shift  $A$   
end while
```

1. What datapath components do we need to perform the computation?
2. How do we control the computation?
3. How do we transfer inputs/outputs?

B&V3, Figure 10.9

ASM chart for the pseudo-code

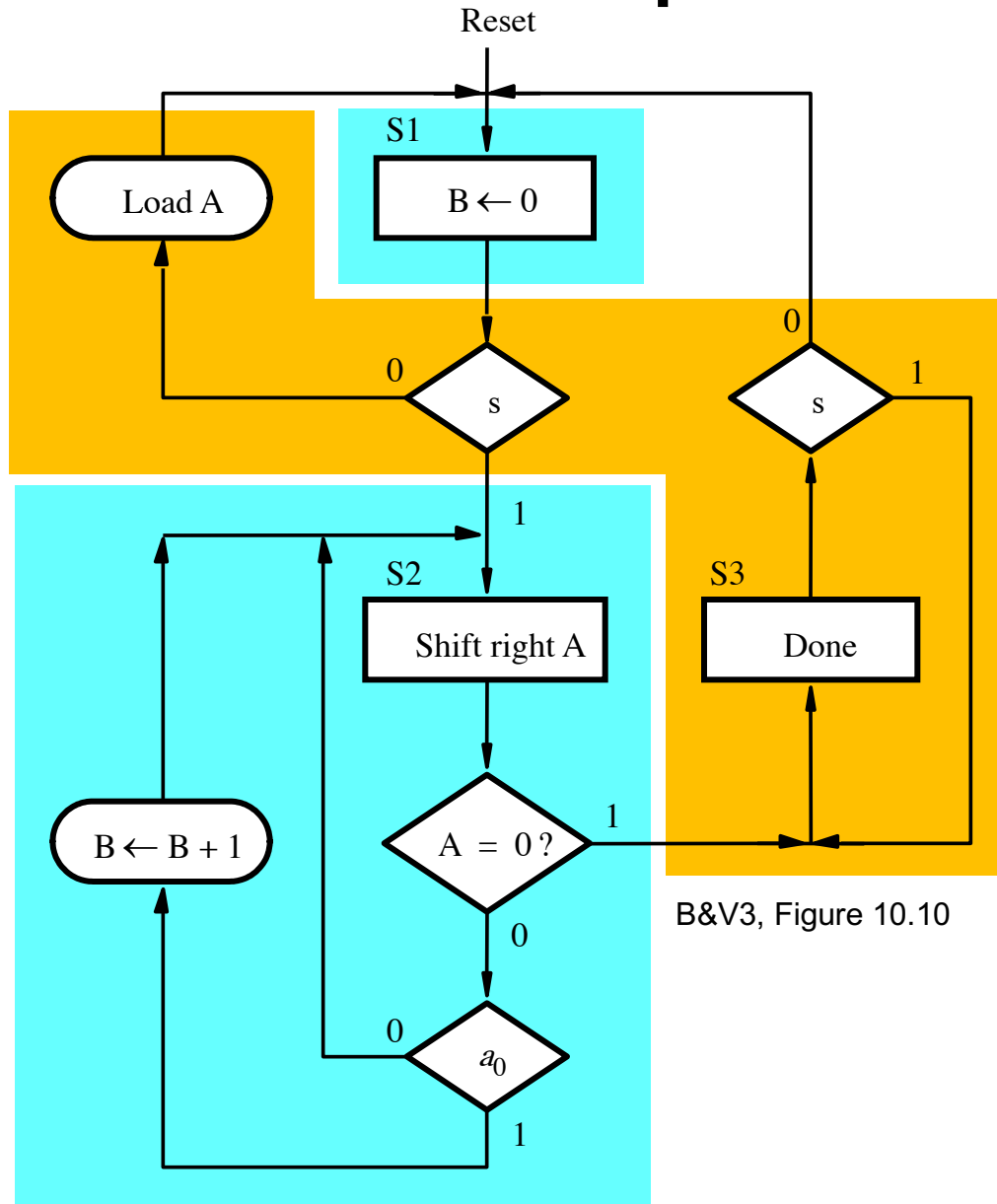

B&V3, Figure 10.10

```


B = 0
while A ≠ 0 do
  if a0 = 1 then
    B = B + 1
  end if
  right shift A
end while
  
```

Note that the ASM chart describes control and datapath aspects of the system in an integrated way

Note use of a “start” signal, s , to indicate when input is available, and a Done signal to indicate when computation has finished
 \Rightarrow handshake protocol used to communicate with the environment or “user” circuit


Take careful note of the state actions – particularly for S2
 \Rightarrow since the “Shift right” action is a Moore-like state output, it won’t occur until the first active clock edge after S2 has been entered, even if that edge causes transition to S3

Datapath for the ASM chart

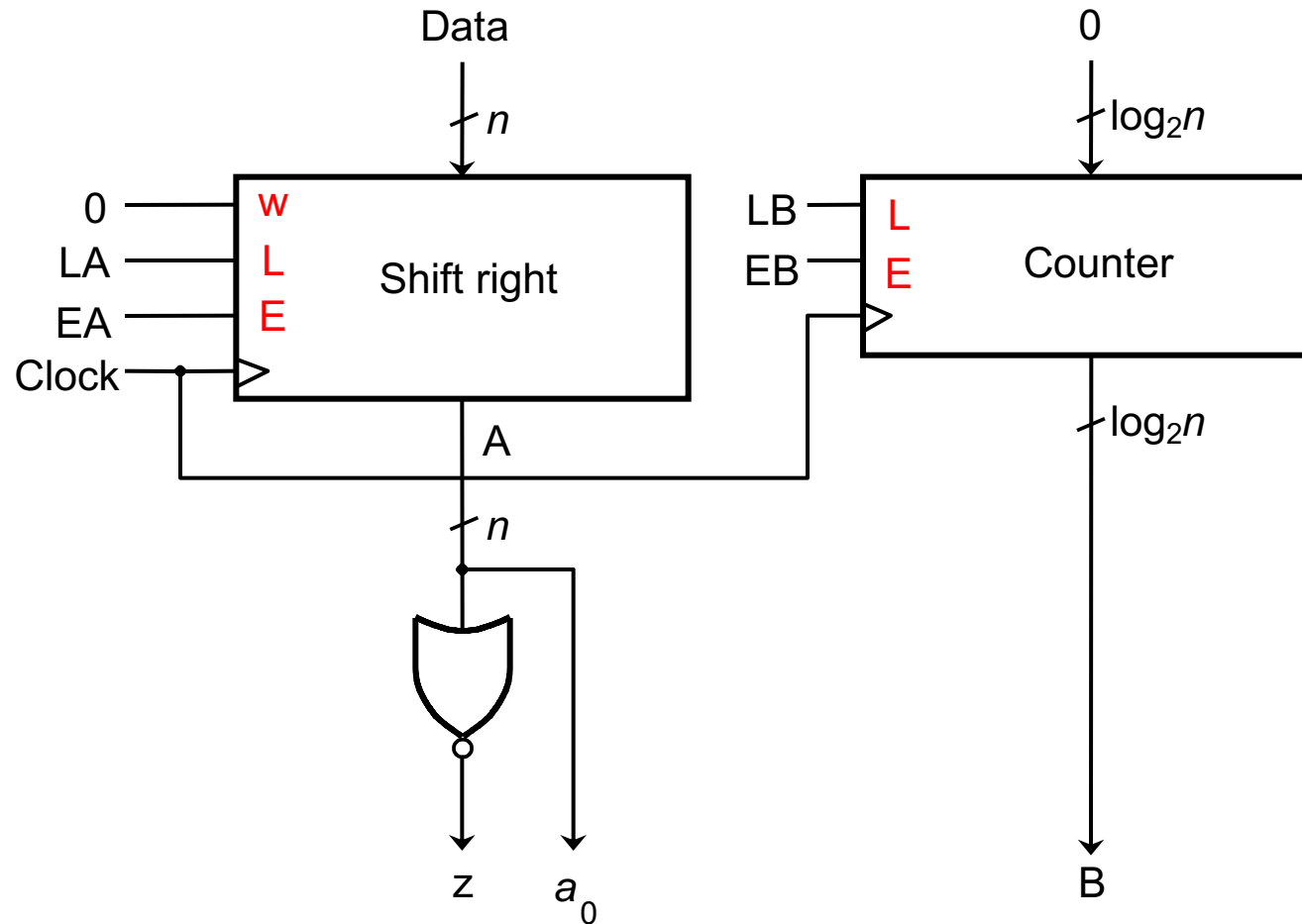


B&V3, Figure 10.11

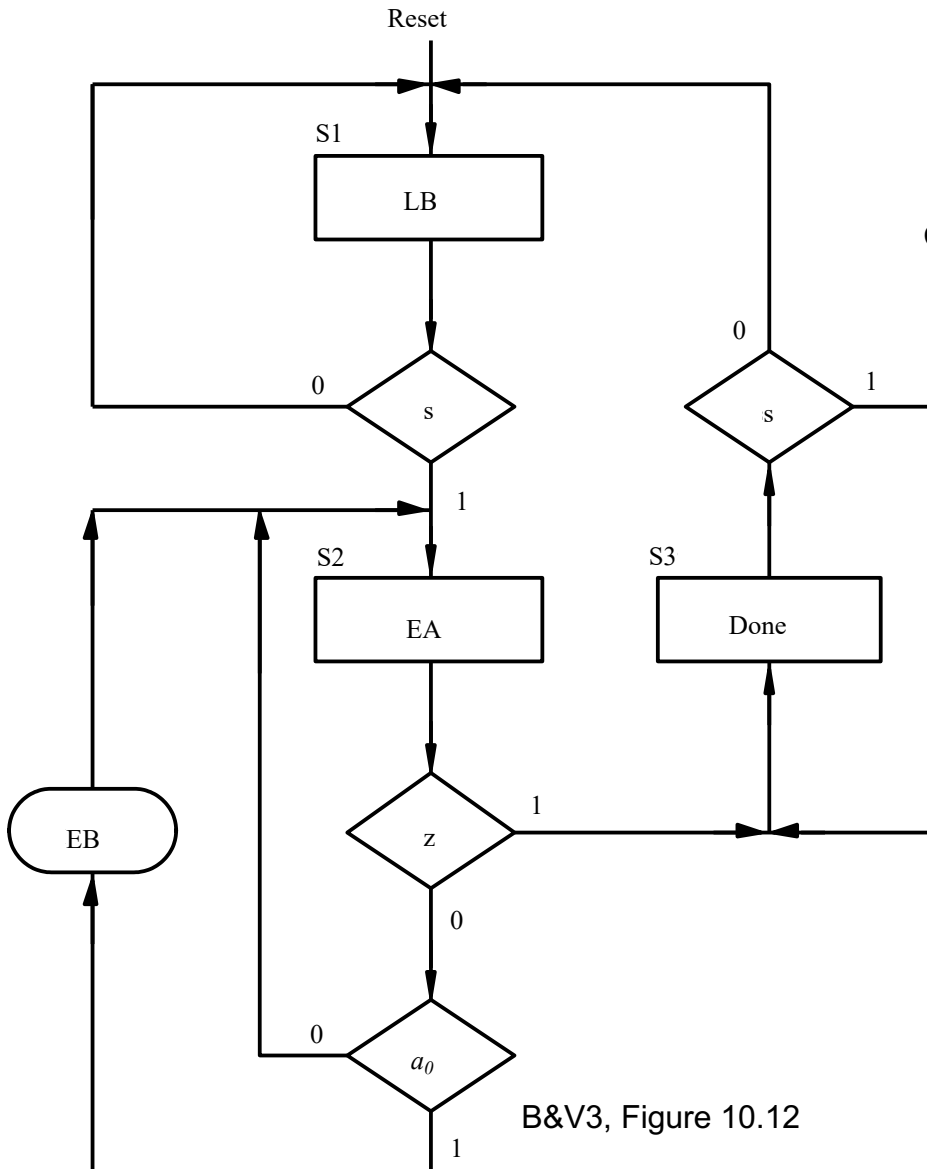ASM chart for the bit counter control circuit



B&V3, Figure 10.12

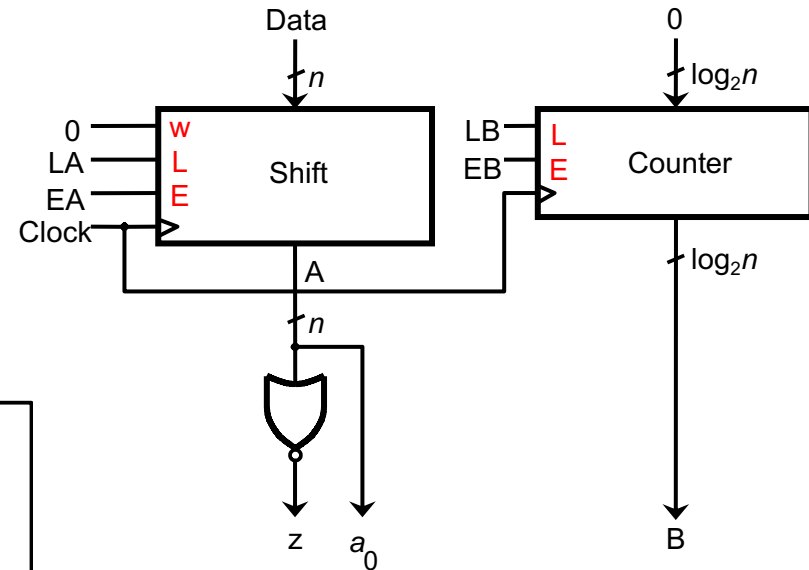

The ASM chart for the pseudocode is refined according to the FSM reqs.

Note: It is assumed that the circuit “user” loads A by asserting LA before asserting the start signal s, and has not completed reading the counter value (after Done is asserted) until after s is deasserted.

VHDL code for the bit-counting circuit (Part a)

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;
USE work.components.shiftrne ;


ENTITY bitcount IS
    PORT( Clock, Resetn    : IN STD_LOGIC ;
          LA, s            : IN STD_LOGIC ;
          Data              : IN
            STD_LOGIC_VECTOR(7 DOWNT0 0) ;
          B                : BUFFER
            INTEGER RANGE 0 to 8 ;
          Done              : OUT STD_LOGIC ) ;
END bitcount ;

```

```

ARCHITECTURE Behavior OF bitcount IS
    TYPE State_type IS ( S1, S2, S3 ) ;
    SIGNAL y : State_type ;
    SIGNAL A : STD_LOGIC_VECTOR(7 DOWNT0 0) ;
    SIGNAL z, EA, LB, EB, low : STD_LOGIC ;

```

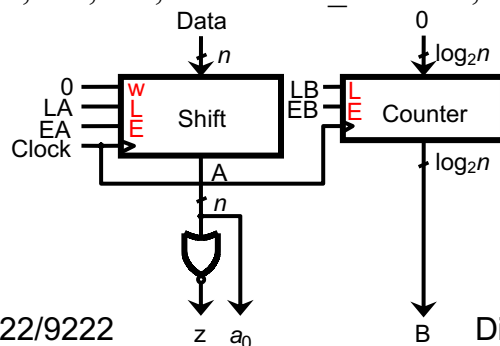


BEGIN

```

FSM_transitions: PROCESS ( Resetn, Clock )
BEGIN
    IF Resetn = '0' THEN
        y <= S1 ;
    ELSIF (Clock'EVENT AND Clock = '1') THEN
        CASE y IS
            WHEN S1 =>
                IF s = '0' THEN y <= S1 ;
                ELSE y <= S2 ; END IF ;
            WHEN S2 =>
                IF z = '0' THEN y <= S2 ;
                ELSE y <= S3 ; END IF ;
            WHEN S3 =>
                IF s = '1' THEN y <= S3 ;
                ELSE y <= S1 ; END IF ;
        END CASE ;
    END IF ;
END PROCESS ;

```

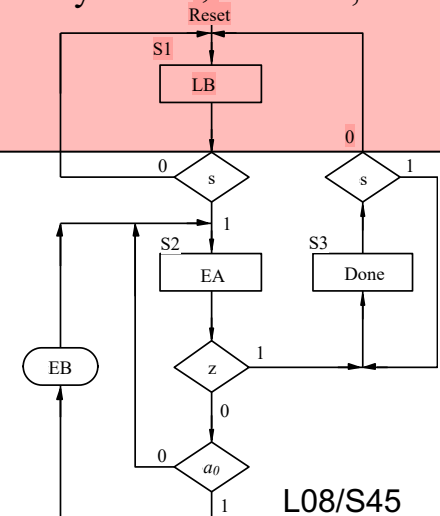... continued in Part b
B&V3, Figure 10.13




VHDL code for the bit-counting circuit (Part *b*)

```

FSM_outputs: PROCESS ( y, A(0) )
BEGIN
    EA <= '0' ; LB <= '0' ; EB <= '0' ; Done <= '0' ;
    CASE y IS
        WHEN S1 =>
            LB <= '1'
        WHEN S2 =>
            EA <= '1' ;
            IF A(0) = '1' THEN EB <= '1' ;
            END IF ;
        WHEN S3 =>
            Done <= '1' ;
    END CASE ;
END PROCESS ;

```

B&V3, Figure 10.13

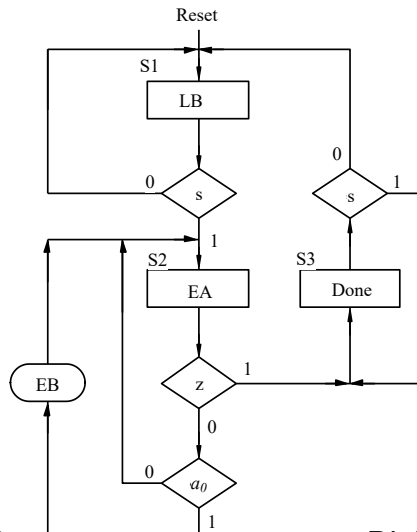


```

-- The datapath circuit is described below
upcount: PROCESS ( Resetn, Clock )
BEGIN
    IF Resetn = '0' THEN
        B <= 0 ;
    ELSIF (Clock'EVENT AND Clock = '1') THEN
        IF LB = '1' THEN
            B <= 0 ;
        ELSIF EB = '1' THEN
            B <= B + 1 ;
        END IF ;
    END IF ;
END PROCESS ;


low <= '0' ;
ShiftA: shiftrne GENERIC MAP ( N => 8 )
    PORT MAP ( Data, LA, EA, low, Clock, A ) ;
z <= '1' WHEN A = "00000000" ELSE '0' ;

```

END Behavior ;

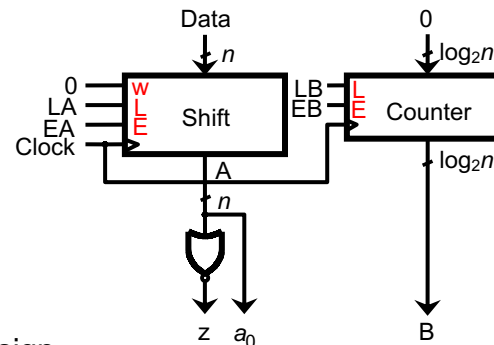


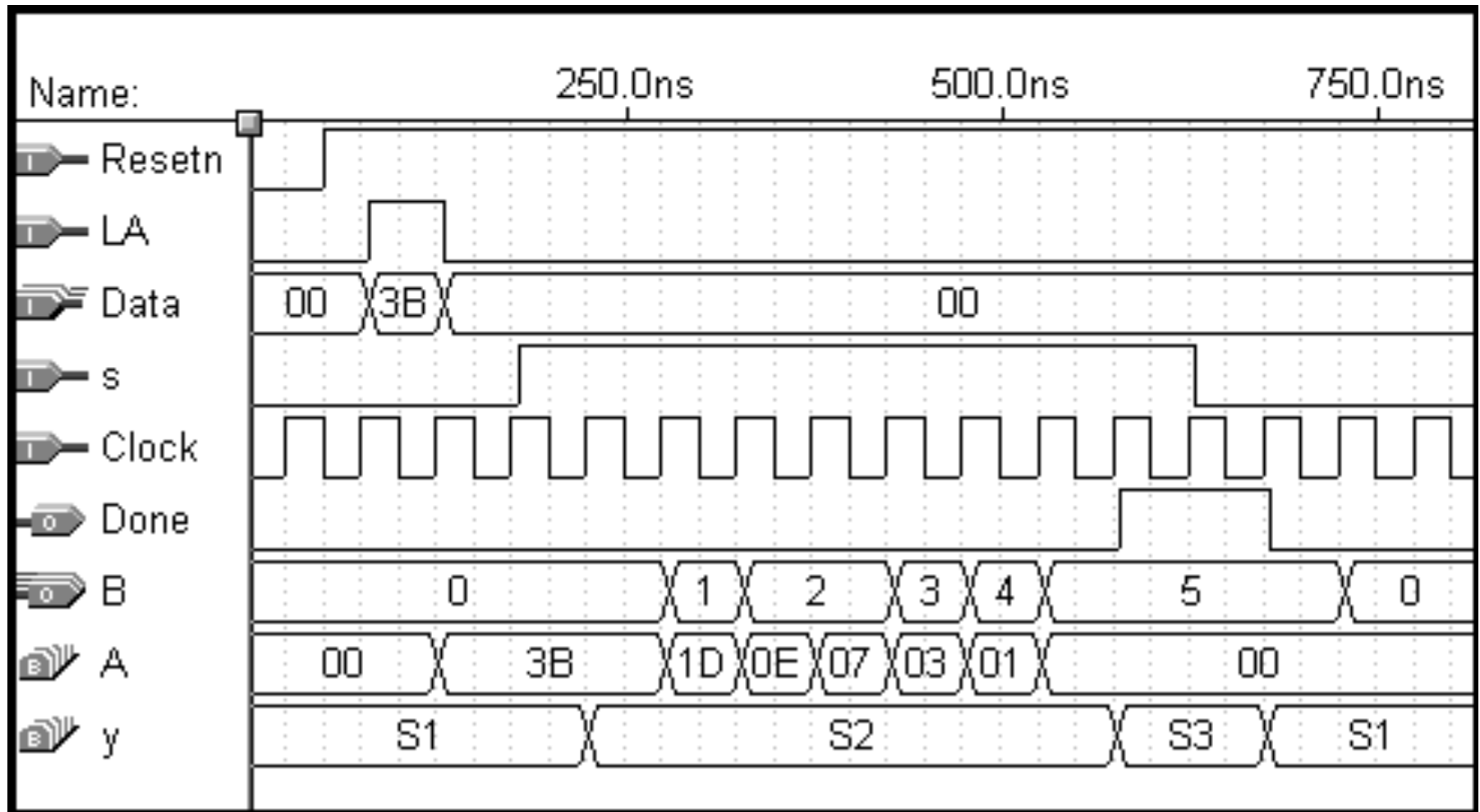Simulation results for the bit-counting circuit




B&V3, Figure 10.14

Practical Issue: Input switch debouncing

 

(a) Single-pole single-throw switch

B&V3, Figure 10.48

 

(b) Single-pole double-throw switch with a basic SR latch

When an input switch is thrown, it can bounce for up to 10ms and thus give rise to an undesirable sequence of pulses on Data.

⇒ One approach to avoiding misreads is to use a latch to trap the switch value.

⇒ **Another is to wait that period before sampling Data.**

Debounce code

synchronise: process (clk)

begin

wait until clk'event and clk = '1';

-- rising clock edge

input_prev <= input_switch;

-- save the current switch setting

-- The following counter counts time that the inputs have been steady

-- The input signal must be steady for approx. 10 milliseconds

if input_switch /= input_prev then

-- if the switch has bounced

sync_count <= (others => '0');

-- reset a counter

elsif sync_count /= x"80000" then

-- otherwise, count ~10ms worth of clock

sync_count <= sync_count + 1;

-- pulses at 50MHz (assumed clock freq.)

end if;

-- If the full time is reached, update the input signals

if sync_count = x"80000" then


input_value <= input_switch;

-- switch has stopped bouncing

end if;

end process synchronise;

Practical Issue: Asynchronous inputs

 


When an asynchronous input fails to satisfy setup or hold times, the flip-flop can enter a metastable state (intermediate/indeterminate value) and not recover for an indefinite period of time.

Using a pair of flip-flops in series significantly reduces the likelihood that any synchronous system reading Data will observe such a metastable value

- COTS (Commercial, Off-The-Shelf) devices typically specify a maximum period of metastability
- as long as the clock period in the circuit above exceeds this value, the FF on the right will not also enter a metastable state even when the FF on the left does
- cost is one clock period of delay or latency in the arrival of the data input

Practical Issue: Clock enable circuit

 


B&V3, Figure 10.43

While seemingly attractive, clock gating to enable a flip-flop is to be avoided as it contributes to clock skew.

Better solution: A flip-flop with an enable input

 It is often desirable to control when a flip-flop or register is loaded with a new value



```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY rege IS
    PORT ( R, Resetn, E, Clock : IN          STD_LOGIC ;
          Q                     : BUFFER     STD_LOGIC ) ;
END rege ;

ARCHITECTURE Behavior OF rege IS
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            Q <= '0' ;
        ELSIF Clock'EVENT AND Clock = '1' THEN
            IF E = '1' THEN
                Q <= R ;
            ELSE
                Q <= Q ;
            END IF ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

B&V3, Figure 10.1

VHDL code for a n -bit register with an enable input


```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY regne IS
    GENERIC ( N : INTEGER := 4 ) ;
    PORT ( R      : IN      STD_LOGIC_VECTOR(N-1 DOWNT0 0) ;
          Resetn  : IN      STD_LOGIC ;
          E, Clock : IN      STD_LOGIC ;
          Q       : OUT     STD_LOGIC_VECTOR(N-1 DOWNT0 0) ) ;
END regne ;

ARCHITECTURE Behavior OF regne IS
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            Q <= (OTHERS => '0') ;
        ELSIF Clock'EVENT AND Clock = '1' THEN
            IF E = '1' THEN
                Q <= R ;
            END IF ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

B&V3, Figure 10.2

 A shift register with parallel-load and enable control inputs



B&V3, Figure 10.3

Code for a right-to-left shift register with an enable input

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

-- right-to-left shift register with parallel load and enable
ENTITY shiftline IS
    GENERIC ( N : INTEGER := 4 ) ;
    PORT( R      : IN      STD_LOGIC_VECTOR(N-1 DOWNT0 0) ;
          L, E, w : IN      STD_LOGIC ;
          Clock   : IN      STD_LOGIC ;
          Q       : BUFFER  STD_LOGIC_VECTOR(N-1 DOWNT0 0) ) ;
END shiftline ;

ARCHITECTURE Behavior OF shiftline IS
BEGIN
    PROCESS
    BEGIN
        WAIT UNTIL Clock'EVENT AND Clock = '1' ;
        IF L = '1' THEN
            Q <= R ;
        ELSIF E = '1' THEN
            Q(0) <= w ;
            Genbits: FOR i IN 1 TO N-1 LOOP
                Q(i) <= Q(i-1) ;
            END LOOP ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

B&V3, Figure 10.4

Component declaration statements assumed for remaining design problems (Part a)

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
```

```
PACKAGE components IS
```

```
-- 2-to-1 multiplexer
```

```
COMPONENT mux2to1
```

```
    PORT ( w0, w1    : IN    STD_LOGIC ;
           s          : IN    STD_LOGIC ;
           f          : OUT   STD_LOGIC ) ;
```

```
END COMPONENT ;
```

```
-- D flip-flop with 2-to-1 multiplexer connected to D
```

```
COMPONENT muxdff
```

```
    PORT ( D0, D1, Sel, Clock : IN    STD_LOGIC ;
           Q                : OUT   STD_LOGIC ) ;
```

```
END COMPONENT ;
```

```
-- n-bit register with enable
```

```
COMPONENT regne
```

```
    GENERIC ( N : INTEGER := 4 ) ;
```

```
    PORT ( R          : IN
           STD_LOGIC_VECTOR(N-1 DOWNT0 0) ;
           Resetn     : IN    STD_LOGIC ;
           E, Clock   : IN    STD_LOGIC ;
           Q           : OUT
           STD_LOGIC_VECTOR(N-1 DOWNT0 0) ) ;
```

```
END COMPONENT ;
```

```
-- n-bit right-to-left shift register with parallel load and enable
```

```
COMPONENT shiftlne -- shift left (towards msb)—mult by 2
```

```
    GENERIC ( N : INTEGER := 4 ) ;
```

```
    PORT ( R          : IN
           STD_LOGIC_VECTOR(N-1 DOWNT0 0) ;
           L, E, w     : IN    STD_LOGIC ;
           Clock       : IN    STD_LOGIC ;
           Q           : BUFFER
           STD_LOGIC_VECTOR(N-1 DOWNT0 0) ) ;
```

```
END COMPONENT ;
```

```
.. continued in Part b
```

B&V3, Figure 10.5

Component declaration statements for digital systems building blocks (Part b)

-- n-bit left-to-right shift register with parallel load and enable

COMPONENT shiftrne -- shift right (towards lsb)—div by 2

 GENERIC (N : INTEGER := 4);

 PORT (R : IN STD_LOGIC_VECTOR(N-1 DOWNT0 0);

 L, E, w : IN STD_LOGIC;

 Clock : IN STD_LOGIC;

 Q : BUFFER STD_LOGIC_VECTOR(N-1 DOWNT0 0));

END COMPONENT;

-- up-counter that counts up from initial value R to modulus-1

COMPONENT upcount

 GENERIC (modulus : INTEGER := 8);

 PORT (Resetn : IN STD_LOGIC;

 Clock, E, L : IN STD_LOGIC;

 R : IN INTEGER RANGE 0 TO modulus-1;

 Q : BUFFER INTEGER RANGE 0 TO modulus-1);

END COMPONENT;

-- down-counter that counts from modulus-1 down to 0

COMPONENT downcnt

 GENERIC (modulus : INTEGER := 8);

 PORT (Clock, E, L : IN STD_LOGIC;

 Q : BUFFER INTEGER RANGE 0 TO modulus-1);

END COMPONENT;

END components ;

B&V3, Figure 10.5

Design Exercise 2:

pp 683 – 692, B&V3

- Implement a binary multiplier circuit

| Decimal | Binary | |
|---------|-----------------|-----------------|
| 13 | 1 1 0 1 | Multiplicand, A |
| 11 | 1 0 1 1 | Multiplier, B |
| <hr/> | <hr/> | |
| 13 | 1 1 0 1 | |
| 13 ↓ | 1 1 0 1 | |
| <hr/> | 0 0 0 0 | |
| 143 | 1 1 0 1 | |
| | <hr/> | |
| | 1 0 0 0 1 1 1 1 | Product, P |

(a) Manual method

```

P = 0
for i = 0 to n-1 do
  if bi = 1 then
    P = P + A
  end if
  left shift A
end for

```

(b) Pseudo-code


B&V3, Figure 10.15

- How is the computation performed?
- What datapath components are required?
- How are they to be controlled?

ASM chart for the multiplier


A: multiplicand
B: multiplier
P: product

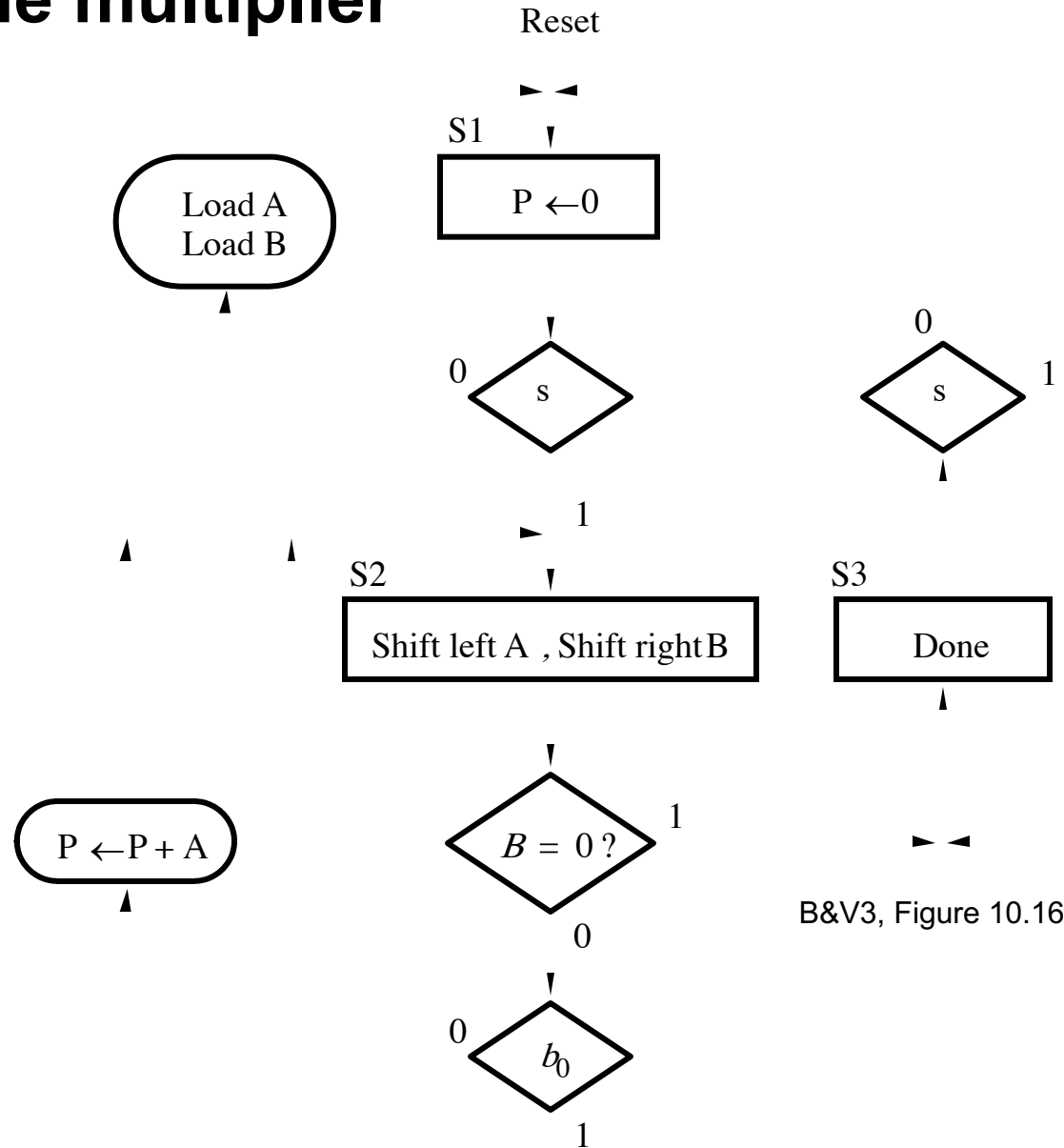$P = 0$
for $i = 0$ to $n-1$ do
 if $b_i = 1$ then
 $P = P + A$
 end if
 left shift A
end for




B&V3, Figure 10.16

Datapath circuit for the multiplier

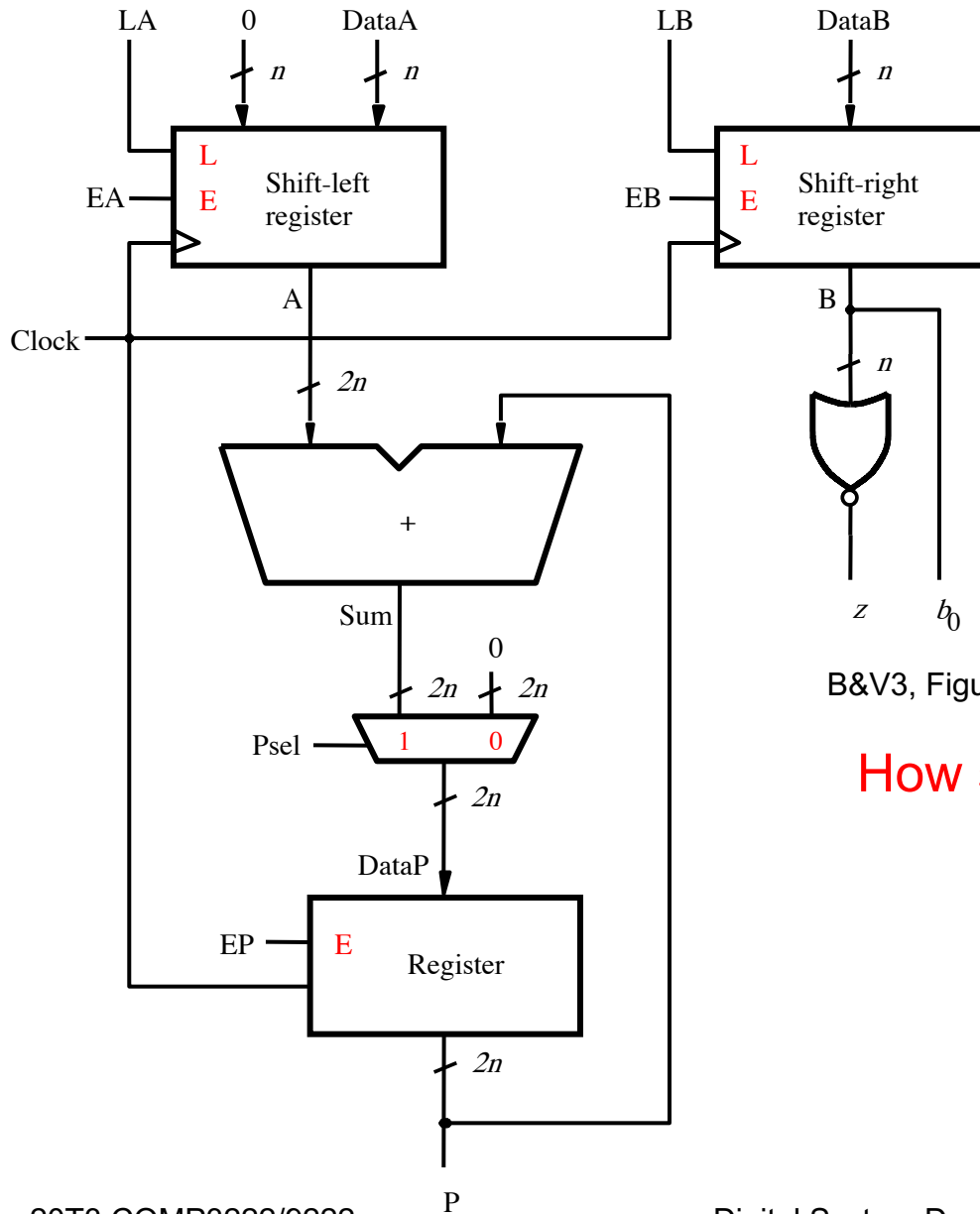


B&V3, Figure 10.17

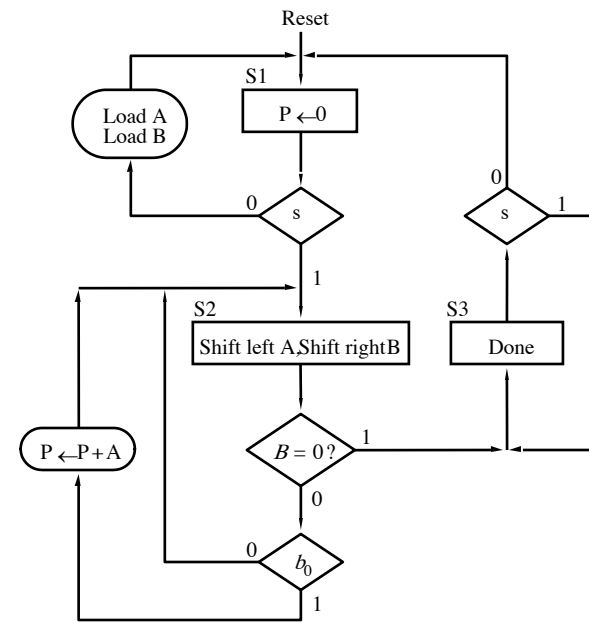

How should the ASM chart be refined?

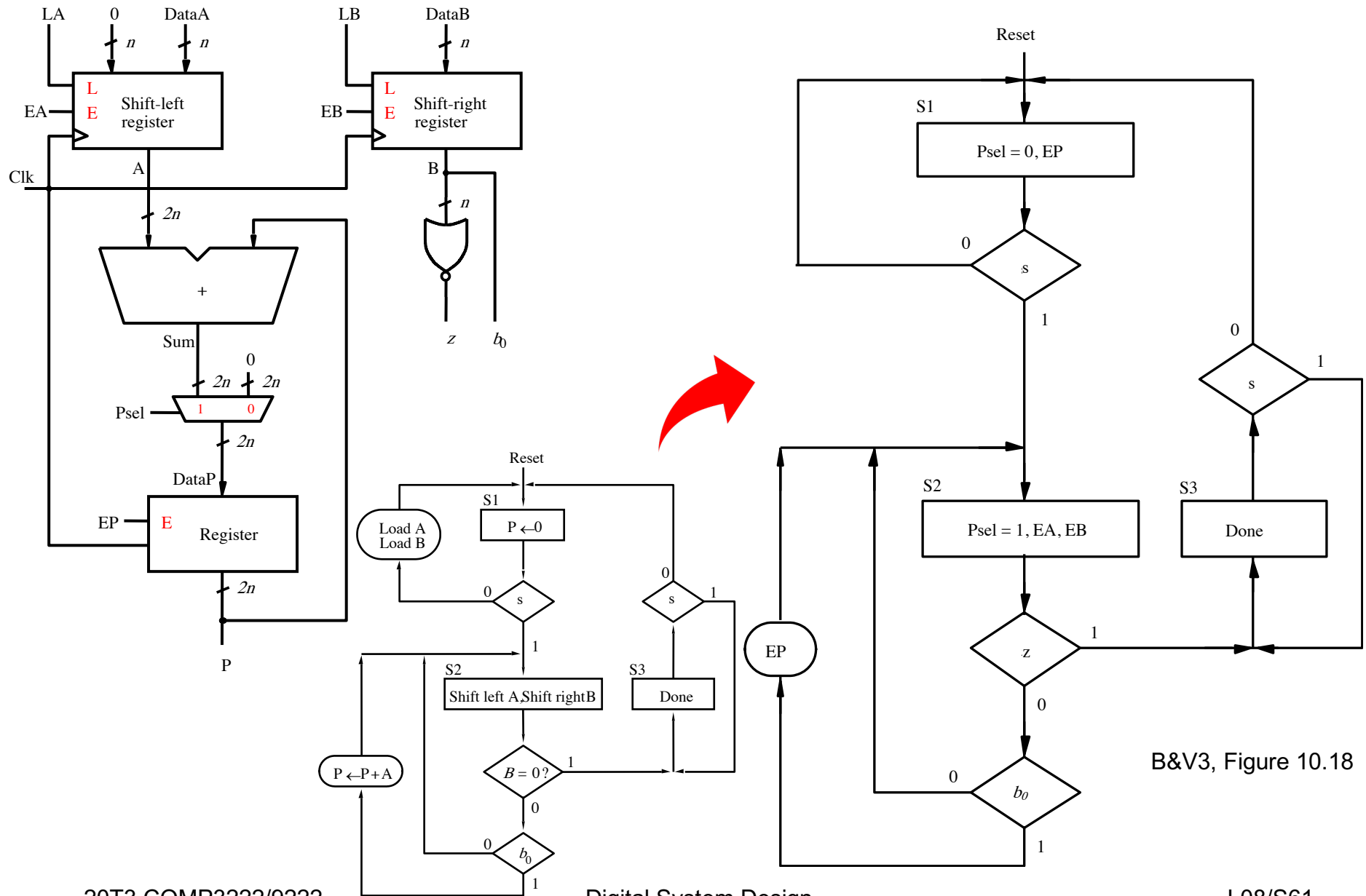ASM chart for the multiplier control circuit



VHDL code for the multiplier circuit (Part a)

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;
USE work.components.all ;

ENTITY multiply IS
    GENERIC ( N : INTEGER := 8; NN : INTEGER := 16 );
    PORT ( Clock      : IN          STD_LOGIC ;
          Resetn      : IN          STD_LOGIC ;
          LA, LB, s    : IN          STD_LOGIC ;
          DataA        : IN          STD_LOGIC_VECTOR(N-1 DOWNT0 0) ;
          DataB        : IN          STD_LOGIC_VECTOR(N-1 DOWNT0 0) ;
          P             : BUFFER     STD_LOGIC_VECTOR(NN-1 DOWNT0 0) ;
          Done         : OUT         STD_LOGIC );
END multiply ;

```

```

ARCHITECTURE Behavior OF multiply IS
    TYPE State_type IS ( S1, S2, S3 );
    SIGNAL y : State_type ;
    SIGNAL Psel, z, EA, EB, EP, Zero : STD_LOGIC ;
    SIGNAL B, N_Zeros : STD_LOGIC_VECTOR(N-1 DOWNT0 0) ;
    SIGNAL A, Ain, DataP, Sum : STD_LOGIC_VECTOR(NN-1 DOWNT0 0) ;
BEGIN

```


B&V3, Figure 10.19

```

FSM_transitions: PROCESS ( Resetn, Clock )
BEGIN
    IF Resetn = '0' THEN
        y <= S1 ;
    ELSIF (Clock'EVENT AND Clock = '1')
    THEN CASE y IS
        WHEN S1 =>
            IF s = '0' THEN y <= S1 ;
            ELSE y <= S2 ; END IF;
        WHEN S2 =>
            IF z = '0' THEN y <= S2 ;
            ELSE y <= S3 ; END IF;
        WHEN S3 =>
            IF s = '1' THEN y <= S3 ;
            ELSE y <= S1 ; END IF;
        END CASE ;
    END IF ;
END PROCESS ;

```

... continued
in Part b

 


VHDL code for the multiplier circuit (Part *b*)

```

FSM_outputs: PROCESS ( y, B(0) )
BEGIN
    EP <= '0' ; EA <= '0' ; EB <= '0' ;
    Done <= '0' ; Psel <= '0';
    CASE y IS
        WHEN S1 =>
            EP <= '1' ;
        WHEN S2 =>
            EA <= '1' ; EB <= '1' ; Psel <= '1' ;
            IF B(0) = '1' THEN EP <= '1' ;
            END IF ;
        WHEN S3 =>
            Done <= '1' ;
    END CASE ;
END PROCESS ;

```

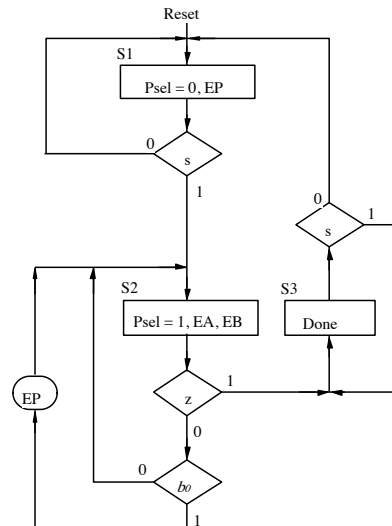


```

-- Define the datapath circuit
Zero <= '0' ;
N_Zeros <= (OTHERS => '0' ) ;
Ain <= N_Zeros & DataA ;
ShiftA: shiftlne GENERIC MAP ( N => NN )
    PORT MAP ( Ain, LA, EA, Zero, Clock, A ) ;
ShiftB: shiftrne GENERIC MAP ( N => N )
    PORT MAP ( DataB, LB, EB, Zero, Clock, B ) ;
z <= '1' WHEN B = N_Zeros ELSE '0' ;
Sum <= A + P ;
-- Define the 2n 2-to-1 multiplexers for DataP
GenMUX: FOR i IN 0 TO NN-1 GENERATE
    Muxi: mux2to1 PORT MAP ( Zero, Sum(i), Psel, DataP(i) ) ;
END GENERATE;
RegP: regne GENERIC MAP ( N => NN )
    PORT MAP ( DataP, Resetn, EP, Clock, P ) ;


```

END Behavior ;

B&V3, Figure 10.19

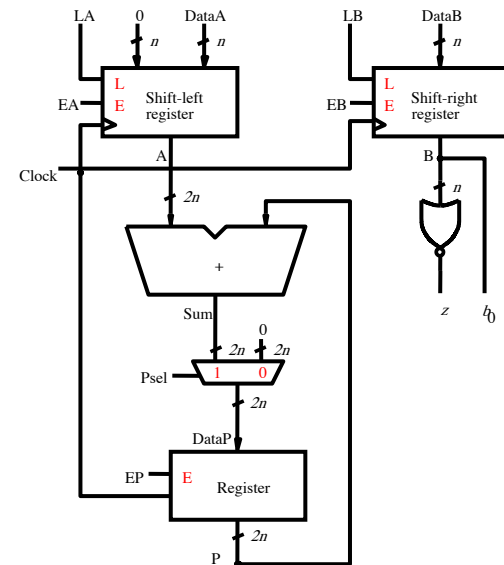

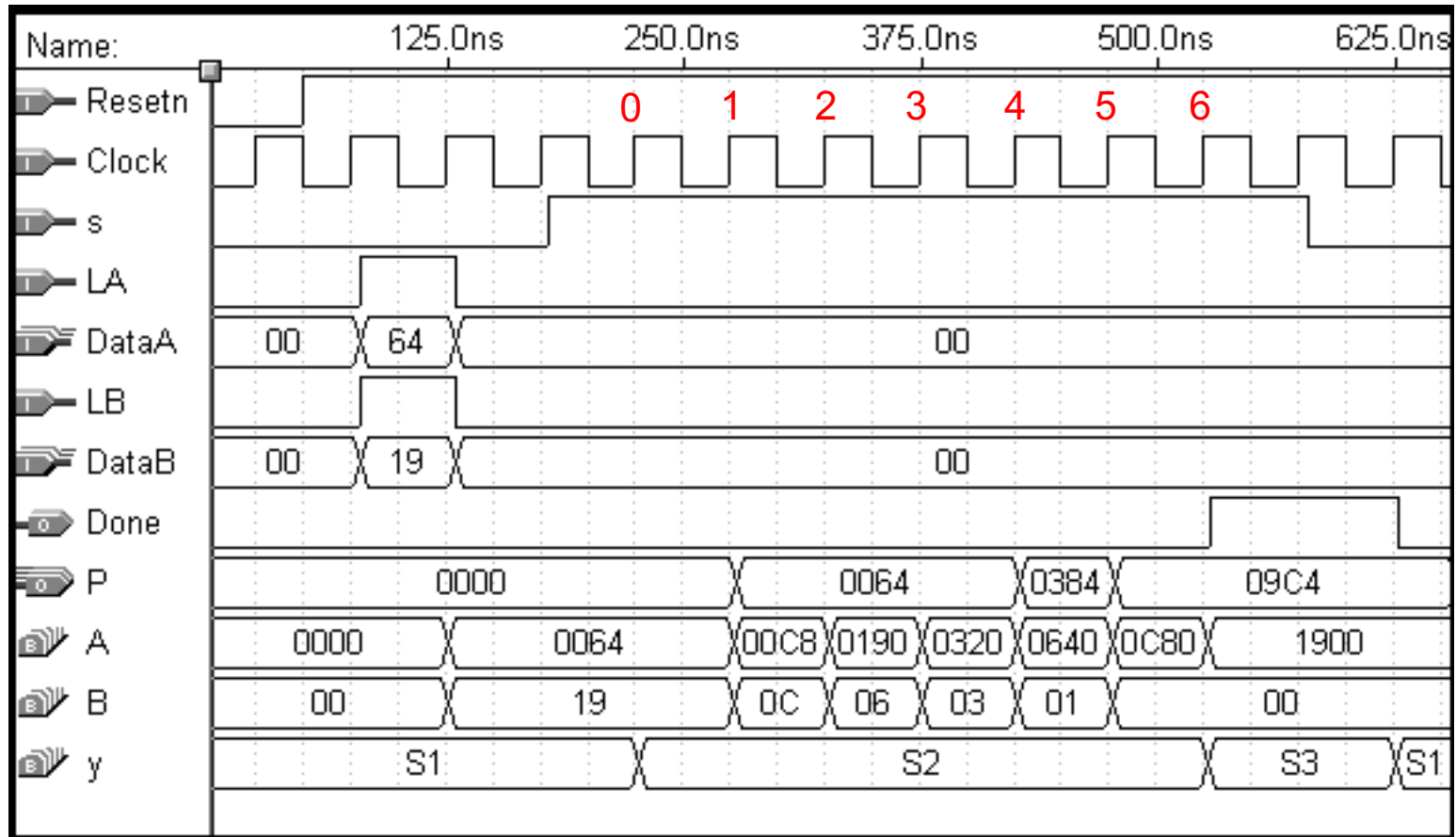Simulation results for the multiplier circuit



B&V3, Figure 10.20

Design Exercise 3: Division

pp 692 – 702, B&V3

$$\begin{array}{r} 15 \\ 9 \overline{) 140} \\ \underline{9} \\ 50 \\ \underline{45} \\ 5 \end{array}$$

(a) An example using decimal numbers

```

R = 0 ;
for i = 0 to n - 1 do
    Left-shift R || A ;
    if R ≥ B then
        qn-1-i = 1 ;
        R = R - B ;
    else
        qn-1-i = 0 ;
    end if;
end for;
    
```

(c) Pseudo-code

B&V3, Figure 10.21

B: Divisor → 1001

$$\begin{array}{r} 00001111 \quad \leftarrow \text{Q: Quotient} \\ 1001 \overline{) 10001100} \quad \leftarrow \text{A: Dividend} \\ \underline{1001} \\ 10001 \\ \underline{1001} \\ 10000 \\ \underline{1001} \\ 1110 \\ \underline{1001} \\ 101 \quad \leftarrow \text{R: Remainder} \end{array}$$


(b) Using binary numbers

1. How is the computation performed?
2. What datapath components are required?
3. How are they to be controlled?

ASM chart for the divider


Answering the question:
How is the computation performed?

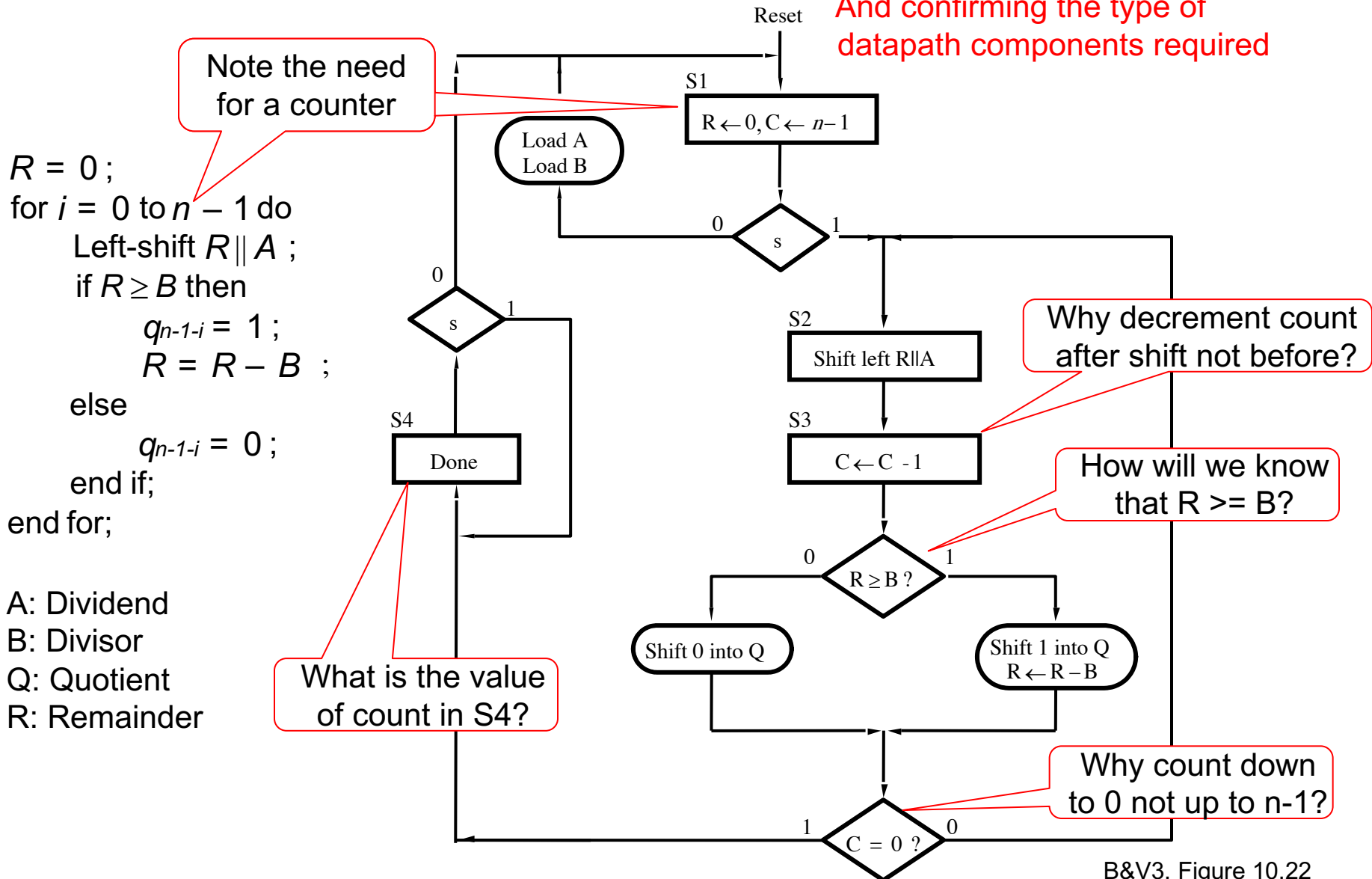And confirming the type of
datapath components required






B&V3, Figure 10.22

Datapath circuit for the divider

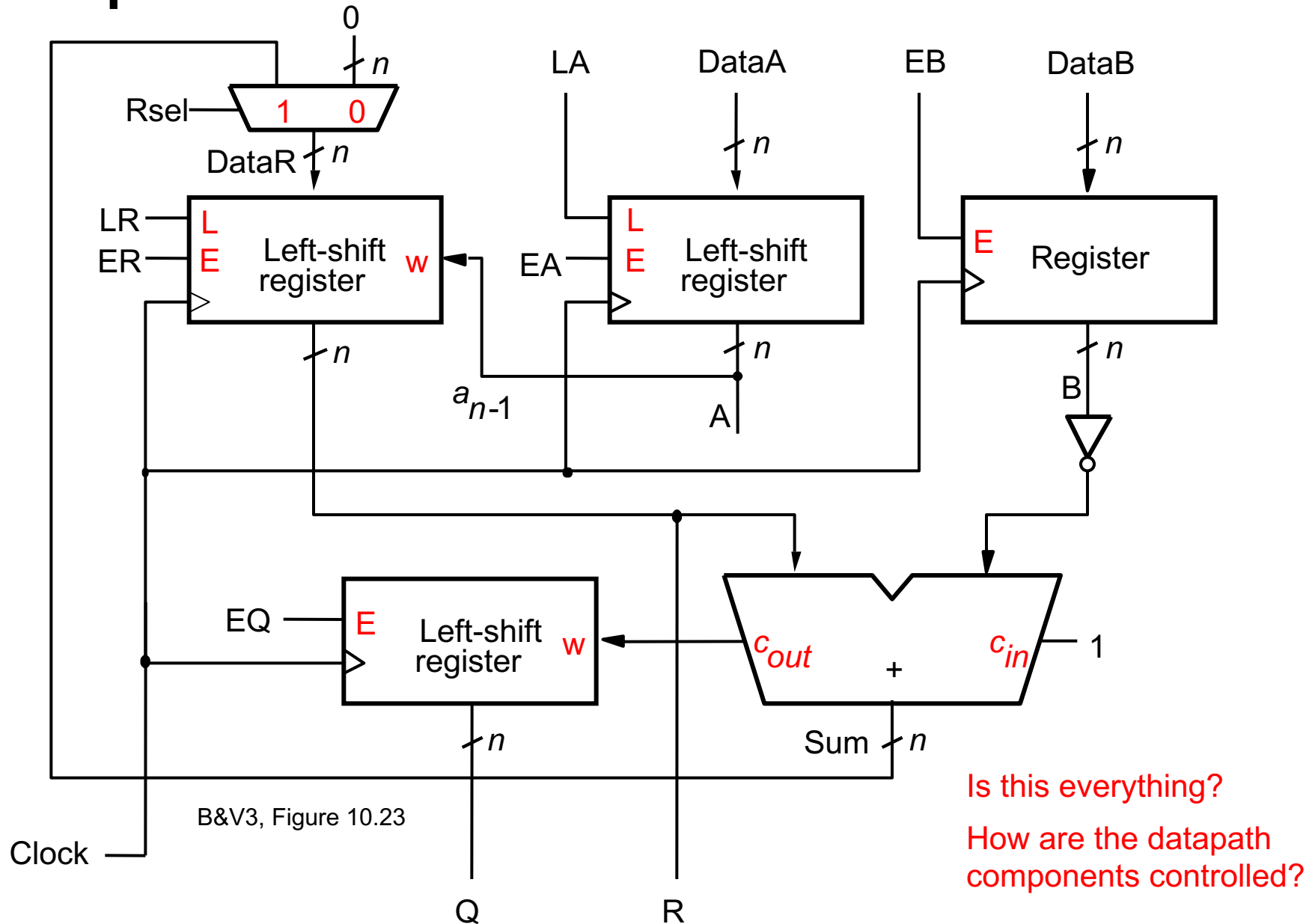

Is this everything?
How are the datapath components controlled?

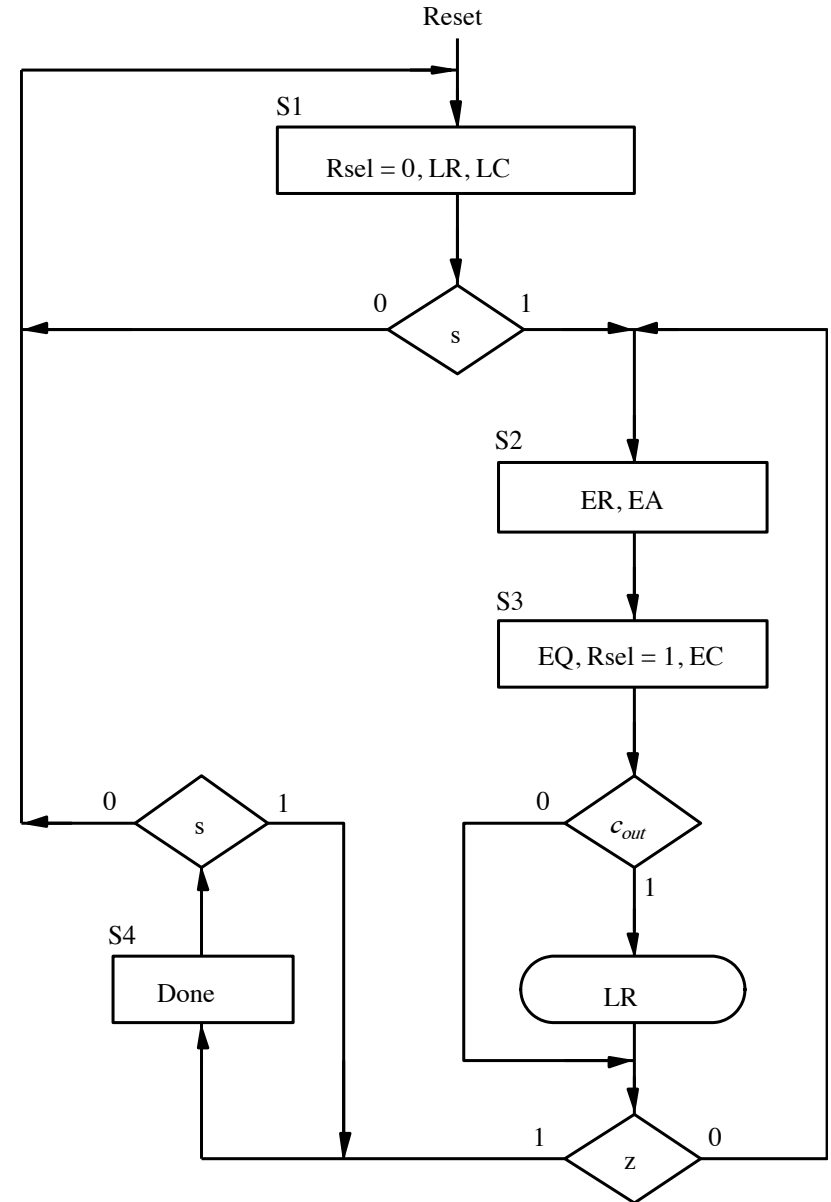 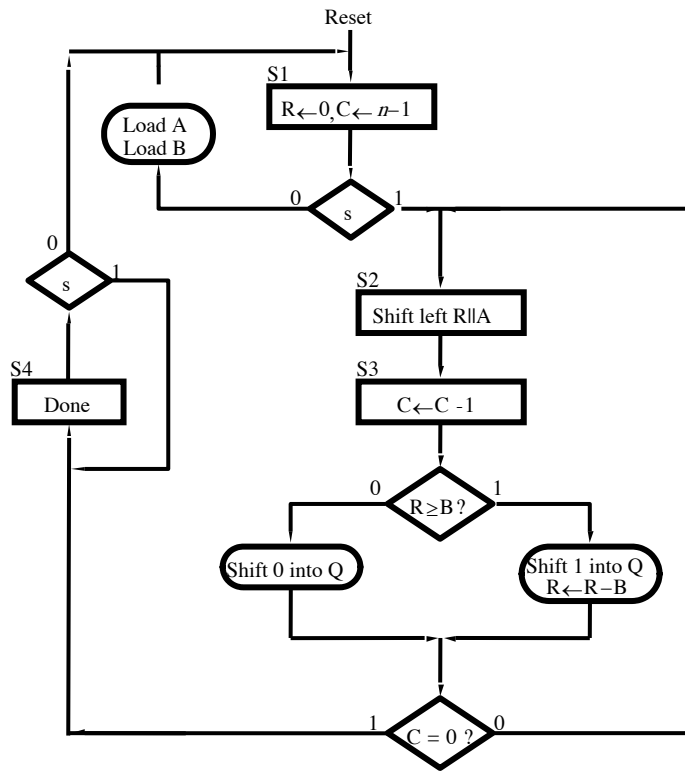ASM chart for the divider control circuit



An example of division using $n = 8$ clk cycles

One drawback of the divider we've designed is that it takes two cycles per iteration to (i) shift $R||A$, and (ii) update $R \leftarrow R - B$ when required.


- A possible enhancement is to perform a shift and a subtraction in a single clock cycle. [write the results of the subtraction to $r_{n-1}..r_0$ | write the new a_{n-1} to a flip-flop, rr_0]
- A second enhancement is to reuse the redundant bits of the shift register for A to store Q.

$$B \rightarrow 1001 \overline{) 10001100} \leftarrow A$$

| Clock cycle | | R | rr ₀ | A/Q |
|-------------|--------------------------------|-----------------|-----------------|-----------------|
| | Load A, B | 0 0 0 0 0 0 0 0 | 0 | 1 0 0 0 1 1 0 0 |
| 0 | Shift left | 0 0 0 0 0 0 0 0 | 1 | 0 0 0 1 1 0 0 0 |
| 1 | Shift left, Q ₀ ← 0 | 0 0 0 0 0 0 0 1 | 0 | 0 0 1 1 0 0 0 0 |
| 2 | Shift left, Q ₀ ← 0 | 0 0 0 0 0 0 1 0 | 0 | 0 1 1 0 0 0 0 0 |
| 3 | Shift left, Q ₀ ← 0 | 0 0 0 0 0 1 0 0 | 0 | 1 1 0 0 0 0 0 0 |
| 4 | Shift left, Q ₀ ← 0 | 0 0 0 0 1 0 0 0 | 1 | 1 0 0 0 0 0 0 0 |
| 5 | Subtract, Q ₀ ← 1 | 0 0 0 0 1 0 0 0 | 1 | 0 0 0 0 0 0 0 1 |
| 6 | Subtract, Q ₀ ← 1 | 0 0 0 0 1 0 0 0 | 0 | 0 0 0 0 0 0 1 1 |
| 7 | Subtract, Q ₀ ← 1 | 0 0 0 0 0 1 1 1 | 0 | 0 0 0 0 0 1 1 1 |
| 8 | Subtract, Q ₀ ← 1 | 0 0 0 0 0 1 0 1 | 0 | 0 0 0 0 1 1 1 1 |

B&V3, Figure 10.25

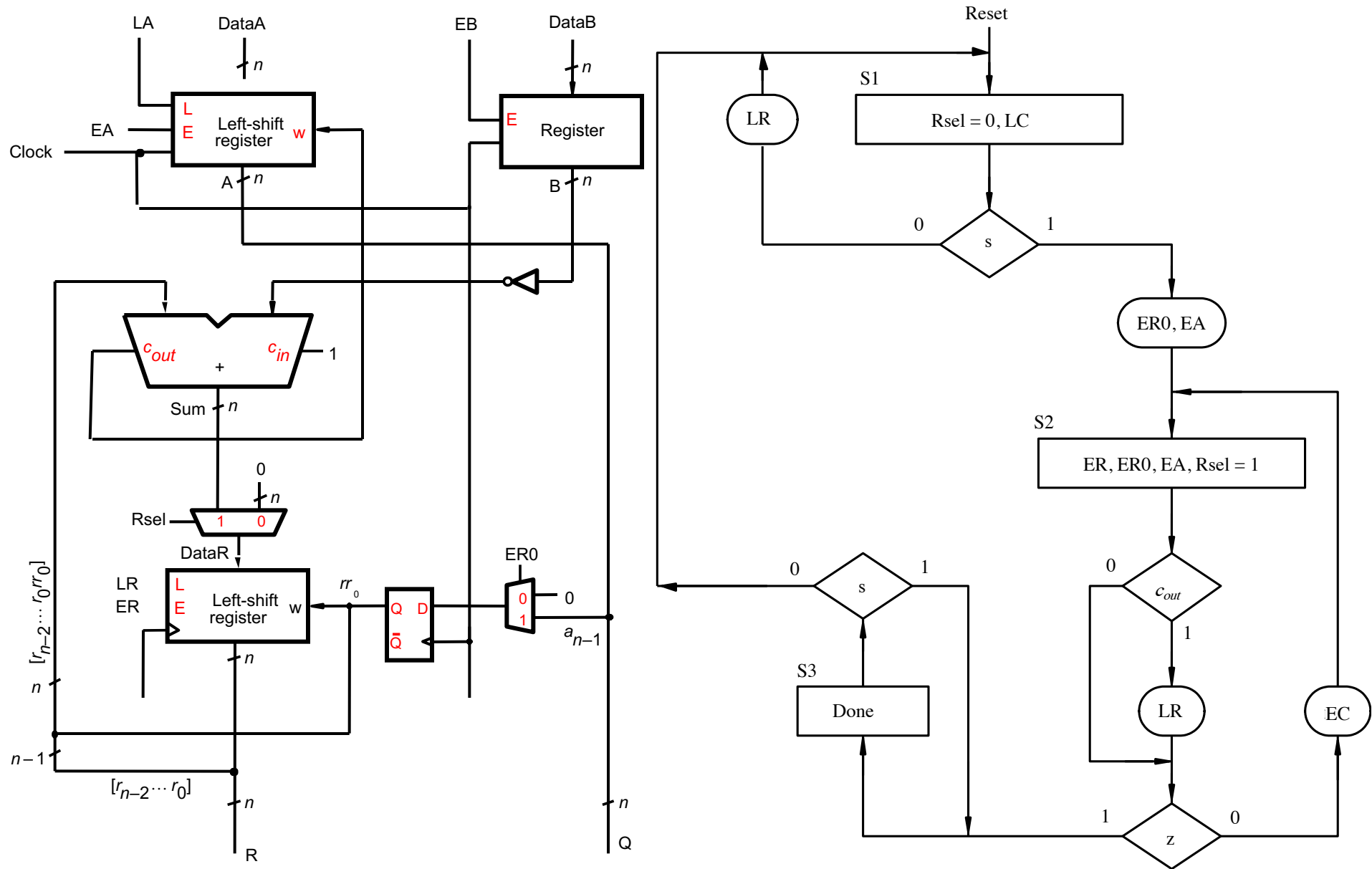ASM chart and datapath circuit for the enhanced divider



VHDL code for the enhanced divider circuit

(Part a)

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_unsigned.all ;
USE work.components.all ;

ENTITY divider IS
    GENERIC ( N : INTEGER := 8 ) ;
    PORT( Clock      : IN          STD_LOGIC ;
          Resetn     : IN          STD_LOGIC ;
          s, LA, EB   : IN          STD_LOGIC ;
          DataA       : IN          STD_LOGIC_VECTOR(N-1 DOWNTO 0) ;
          DataB       : IN          STD_LOGIC_VECTOR(N-1 DOWNTO 0) ;
          R, Q        : BUFFER STD_LOGIC_VECTOR(N-1 DOWNTO 0) ;
          Done        : OUT         STD_LOGIC ) ;
END divider ;
```

B&V3, Figure 10.28

VHDL code for the enhanced divider circuit (Part b)

```


ARCHITECTURE Behavior OF divider IS
  TYPE State_type IS ( S1, S2, S3 );
  SIGNAL y : State_type;
  SIGNAL Zero, Cout, z : STD_LOGIC;
  SIGNAL EA, Rsel, LR, ER, ER0, LC, EC, R0 : STD_LOGIC;
  SIGNAL A, B, DataR : STD_LOGIC_VECTOR(N-1 DOWNT0 0);
  SIGNAL Sum : STD_LOGIC_VECTOR(N DOWNT0 0);
  SIGNAL Count : INTEGER RANGE 0 TO N-1;
BEGIN

```

```

  FSM_transitions: PROCESS ( Resetn, Clock )
  BEGIN
    IF Resetn = '0' THEN y <= S1;
    ELSIF (Clock'EVENT AND Clock = '1') THEN
      CASE y IS
        WHEN S1 =>
          IF s = '0' THEN y <= S1; ELSE y <= S2; END IF;
        WHEN S2 =>
          IF z = '0' THEN y <= S2; ELSE y <= S3; END IF;
        WHEN S3 =>
          IF s = '1' THEN y <= S3; ELSE y <= S1; END IF;
      END CASE;
    END IF;
  END PROCESS;

```

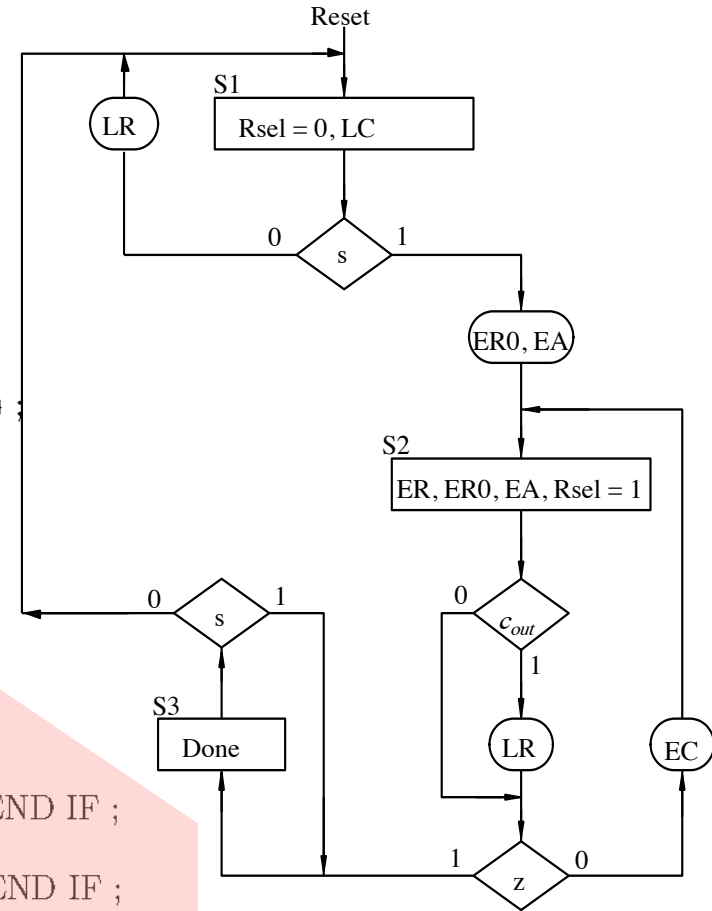

B&V3, Figure 10.28

VHDL code for the enhanced divider circuit

(Part c)

```
FSM_outputs: PROCESS ( s, y, Cout, z )
```

```
BEGIN
```

```
  LR <= '0' ; ER <= '0' ; ER0 <= '0' ;
```

```
  LC <= '0' ; EC <= '0' ; EA <= '0' ; Done <= '0' ;
```

```
  Rsel <= '0' ;
```

```
  CASE y IS
```

```
    WHEN S1 =>
```

```
      LC <= '1' ;
```

```
      IF s = '0' THEN
```

```
        LR <= '1' ; EA <= '0' ; ER0 <= '0' ;
```

```
      ELSE
```

```
        LR <= '0' ; EA <= '1' ; ER0 <= '1' ;
```

```
      END IF ;
```

```
    WHEN S2 =>
```

```
      Rsel <= '1' ; ER <= '1' ; ER0 <= '1' ; EA <= '1' ;
```

```
      IF Cout = '1' THEN LR <= '1' ; ELSE LR <= '0' ; END IF ;
```

```
      IF z = '0' THEN EC <= '1' ; ELSE EC <= '0' ; END IF ;
```


```
    WHEN S3 =>
```

```
      Done <= '1' ;
```

```
  END CASE ;
```

```
END PROCESS ;
```

B&V3, Figure 10.28

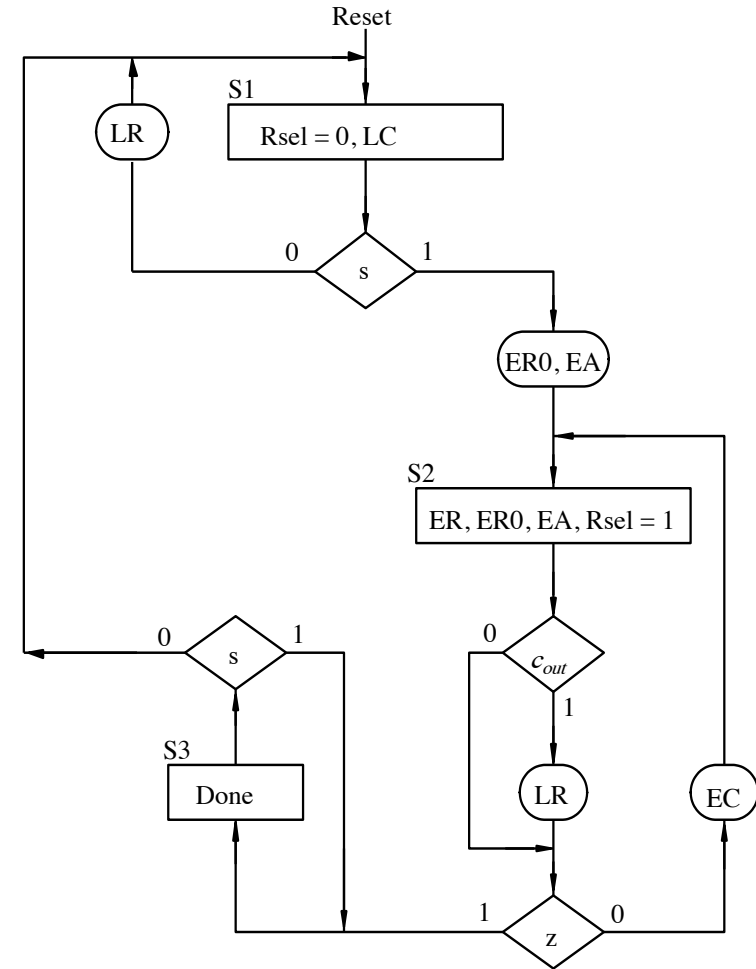


VHDL code for the enhanced divider circuit (Part d)

```
-- define the datapath circuit
Zero <= '0' ;
RegB: regne GENERIC MAP ( N => N )
  PORT MAP ( DataB, Resetn, EB, Clock, B ) ;
ShiftR: shiftlne GENERIC MAP ( N => N )
  PORT MAP ( DataR, LR, ER, R0, Clock, R ) ;
FF_R0: muxdff PORT MAP ( Zero, A(N-1), ER0, Clock, R0 ) ;
ShiftA: shiftlne GENERIC MAP ( N => N )
  PORT MAP ( DataA, LA, EA, Cout, Clock, A ) ;
Q <= A ;
Counter: downcnt GENERIC MAP ( modulus => N )
  PORT MAP ( Clock, EC, LC, Count ) ;
z <= '1' WHEN Count = 0 ELSE '0' ;


Sum <= R & R0 + (NOT B +1) ;
Cout <= Sum(N) ;
DataR <= (OTHERS => '0') WHEN Rsel = '0' ELSE Sum ;
```

END Behavior ;

B&V3, Figure 10.28

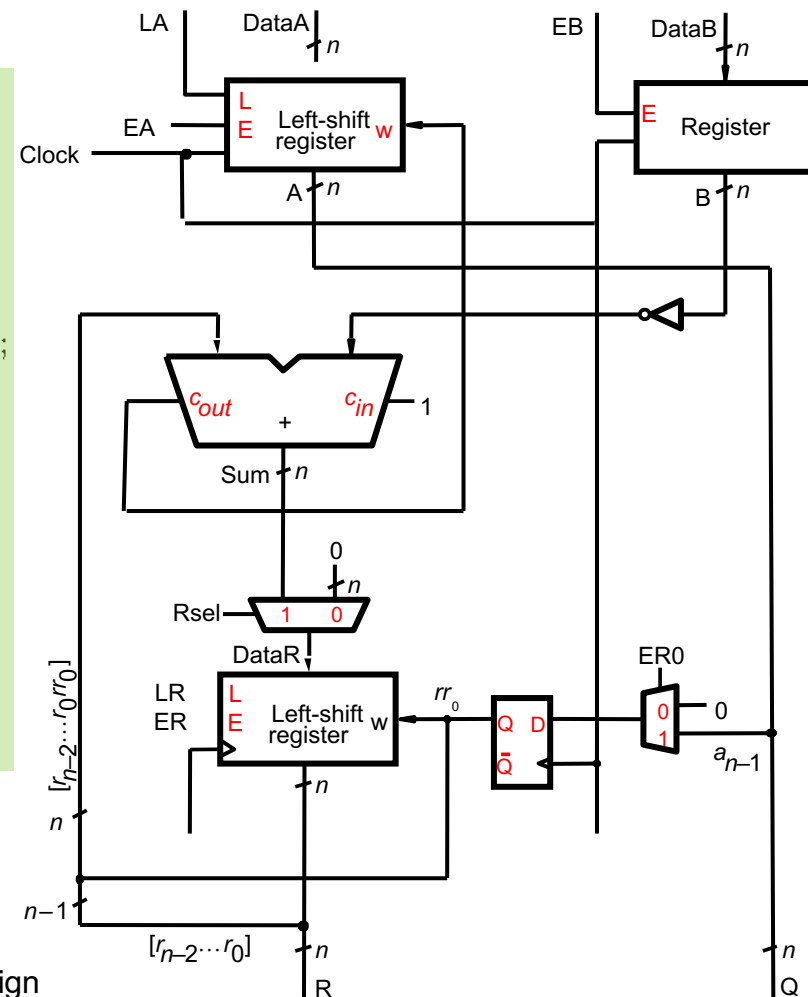

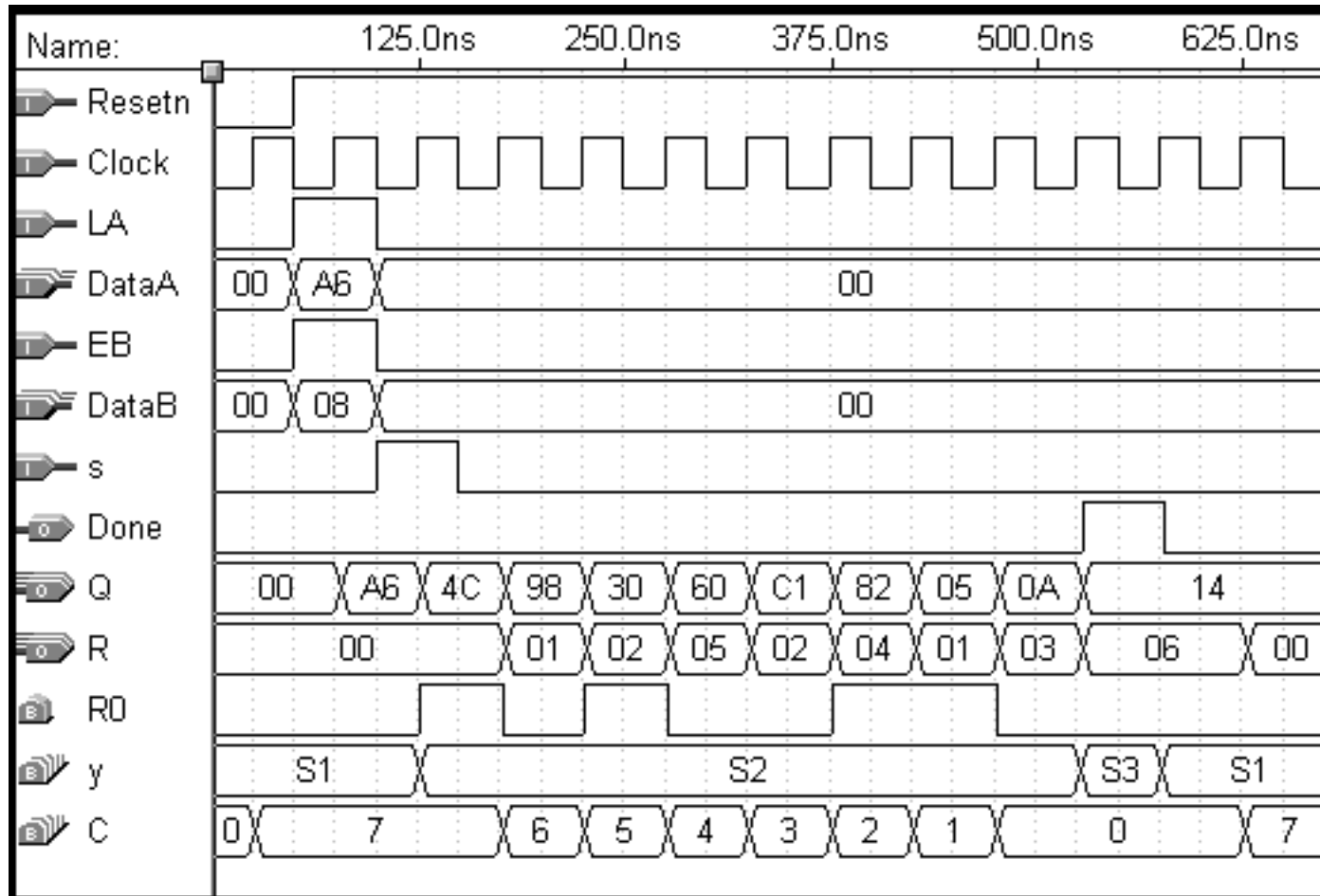Simulation results for the enhanced divider circuit




B&V3, Figure 10.29

Design Ex 4: Finding the mean of k numbers

pp 702 – 708, B&V3

```
Sum = 0 ;  
for  $i = k - 1$  downto 0 do  
    Sum = Sum +  $R_i$  ;  
endfor;  
 $M = \text{Sum} \div k$  ;
```


(a) Pseudo-code

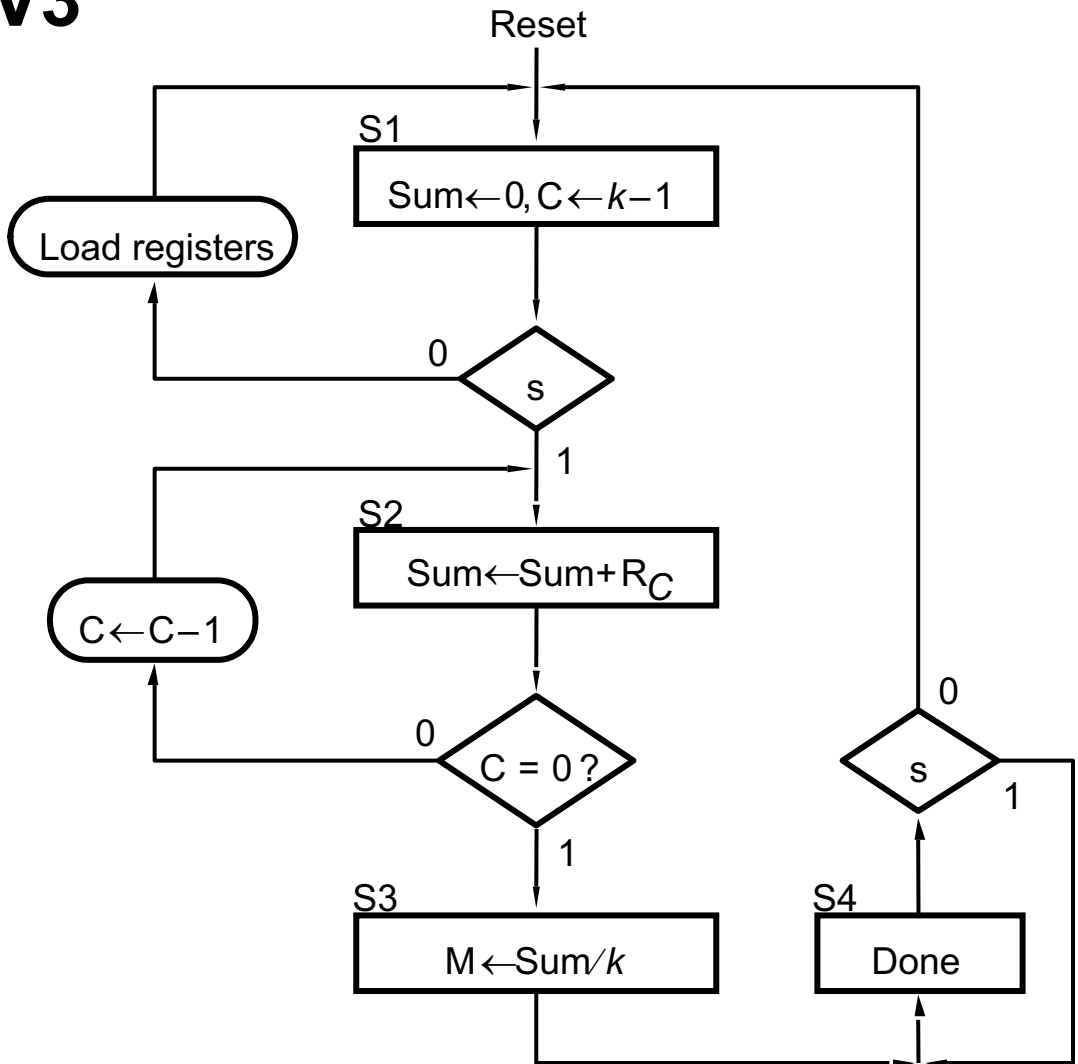

(b) ASM chart


B&V3, Figure 10.30

Finding the mean of k numbers – datapath


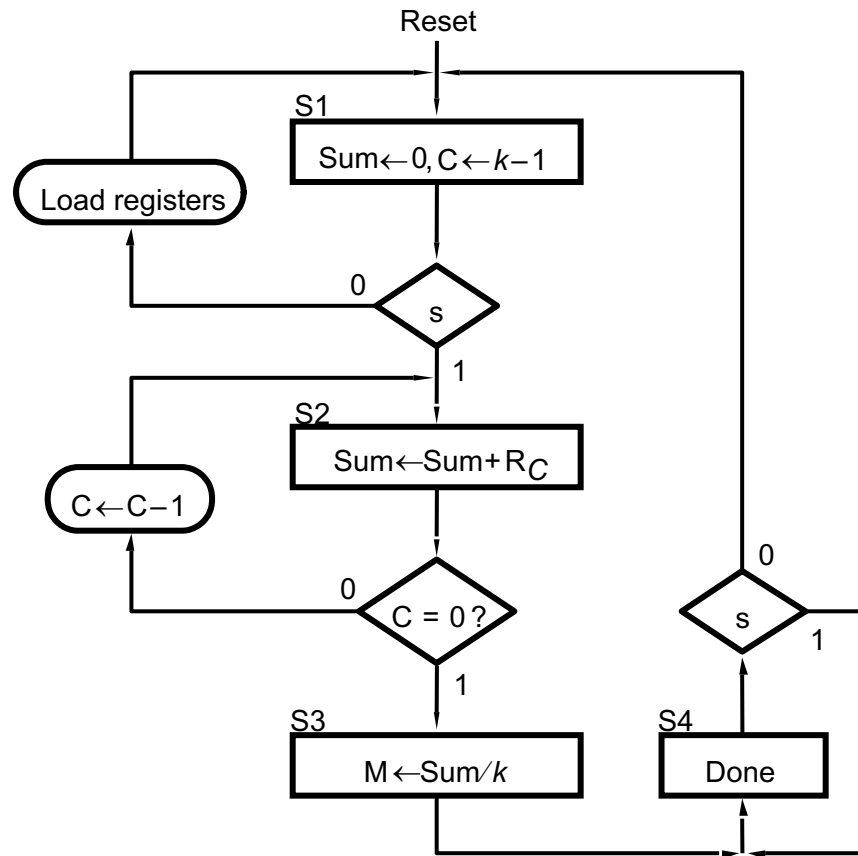


(b) ASM chart


B&V3, Figure 10.30

 

B&V3, Figure 10.31

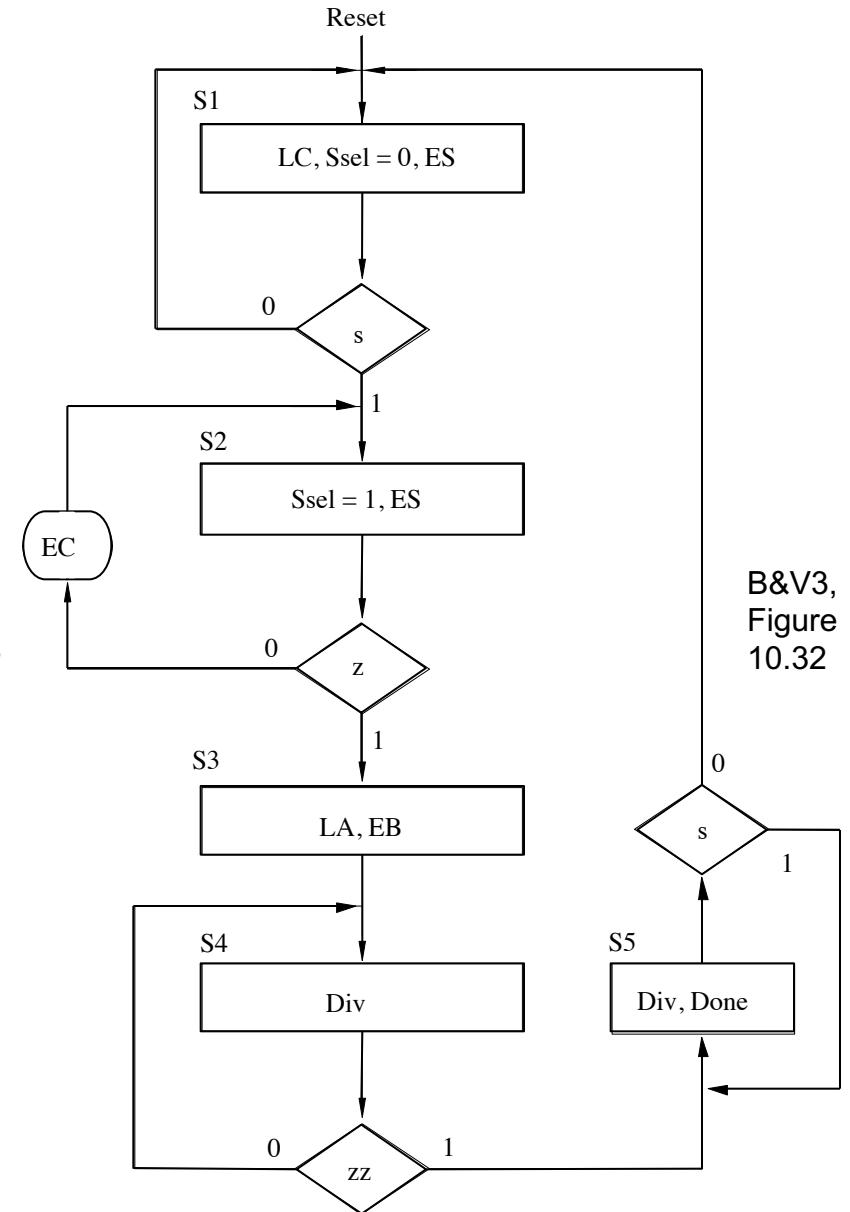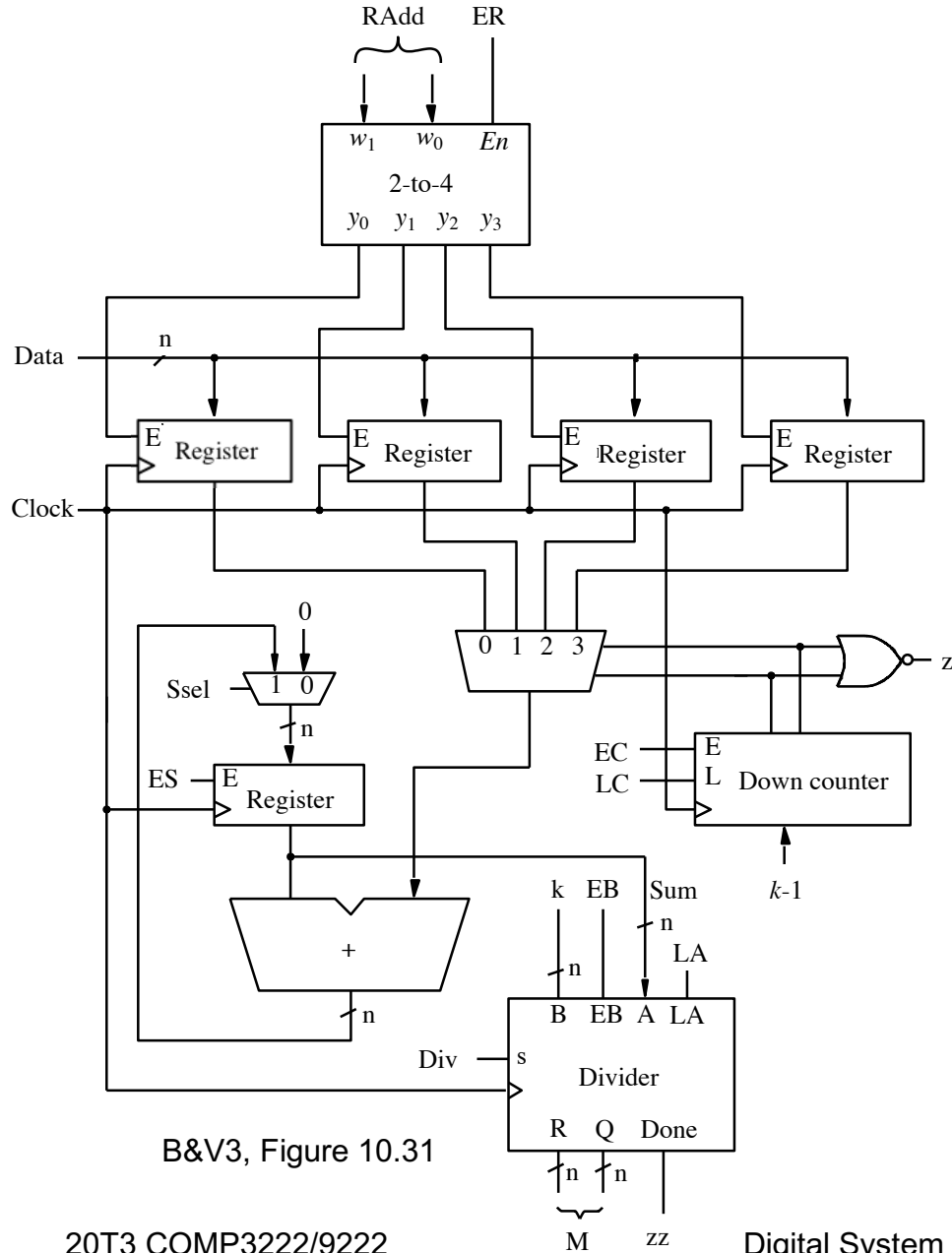

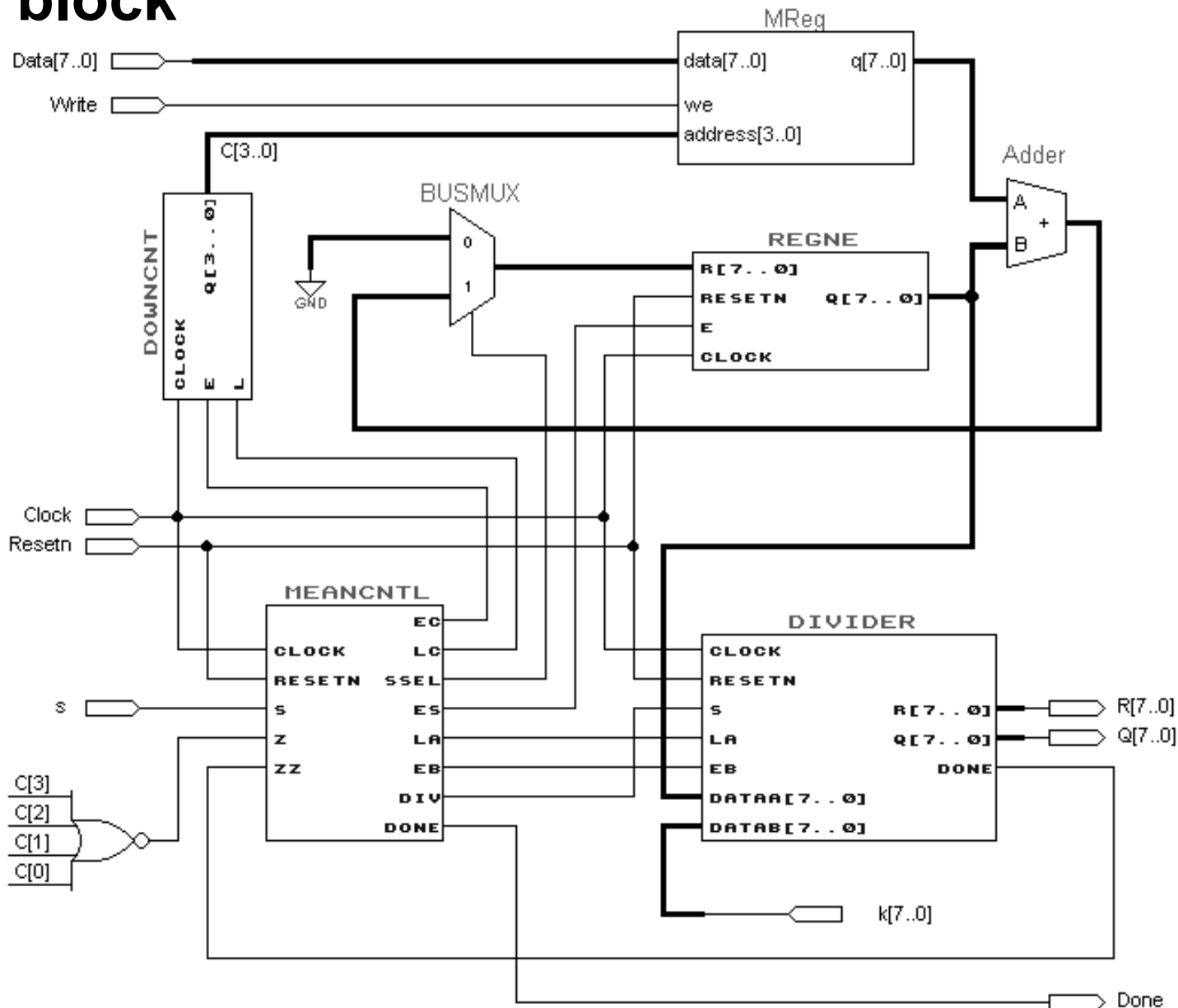
Schematic of the mean circuit with an SRAM block



B&V3, Figure 10.33

Simulation results for the mean circuit using SRAM

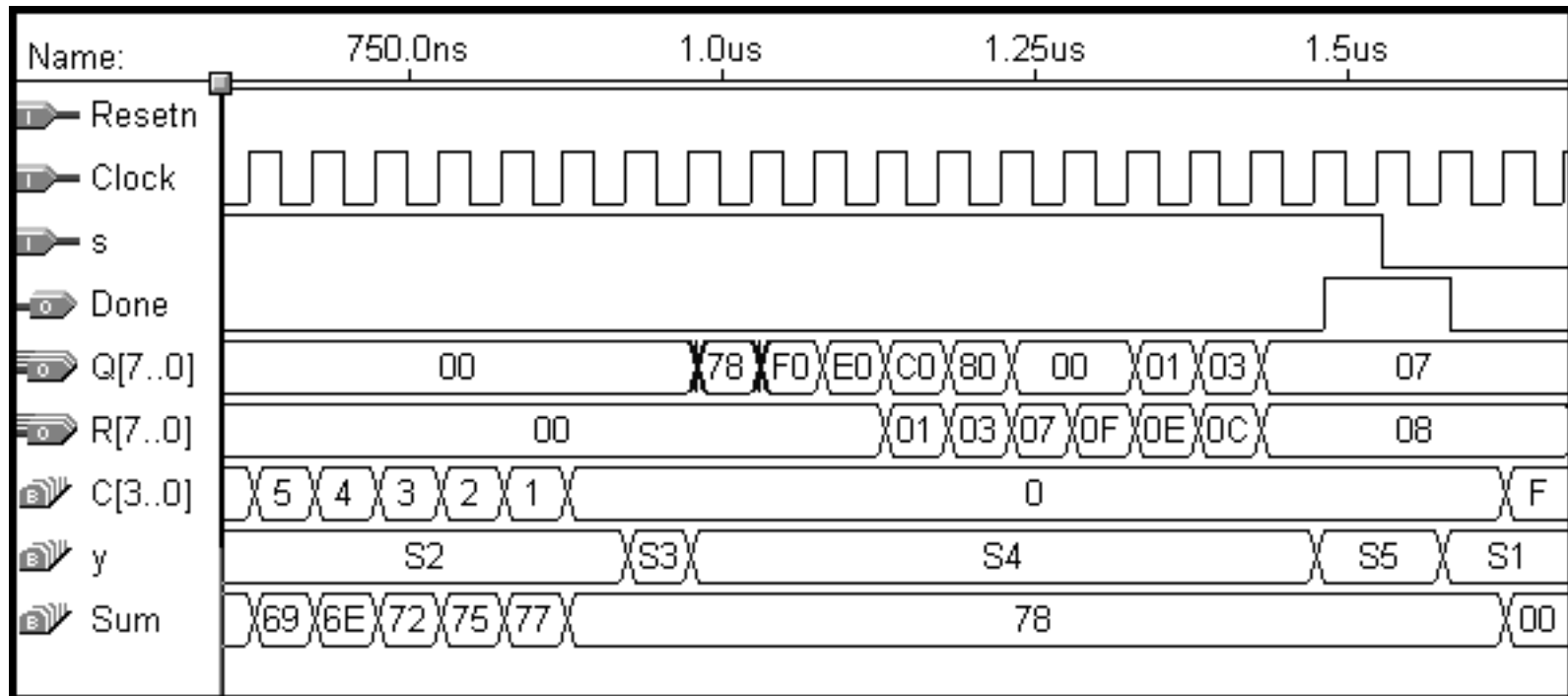Results are for finding the mean of numbers 0..15



B&V3, Figure 10.34

Design Ex 5: Sort k words

pp 708 – 718, B&V3

```
// bubblesort
for  $i = 0$  to  $k-2$  do
   $A = R_i$ ;
  for  $j = i+1$  to  $k-1$  do
     $B = R_j$ ;
    if  $B < A$  then
       $R_j = A$ ;
       $R_i = B$ ; // place smallest of  $[i+1, k-1]$  in  $R_i$ 
       $A = R_i$ ;
    end if;
  end for;
end for;
```


B&V3, Figure 10.35

ASM chart for the sort operation

```


for  $i = 0$  to  $k-2$  do
   $A = R_i$ ;
  for  $j = i+1$  to  $k-1$  do
     $B = R_j$ ;
    if  $B < A$  then
       $R_j = A$ ;
       $R_i = B$ ;
       $A = R_i$ ;
    end if;
  end for;
end for;

```

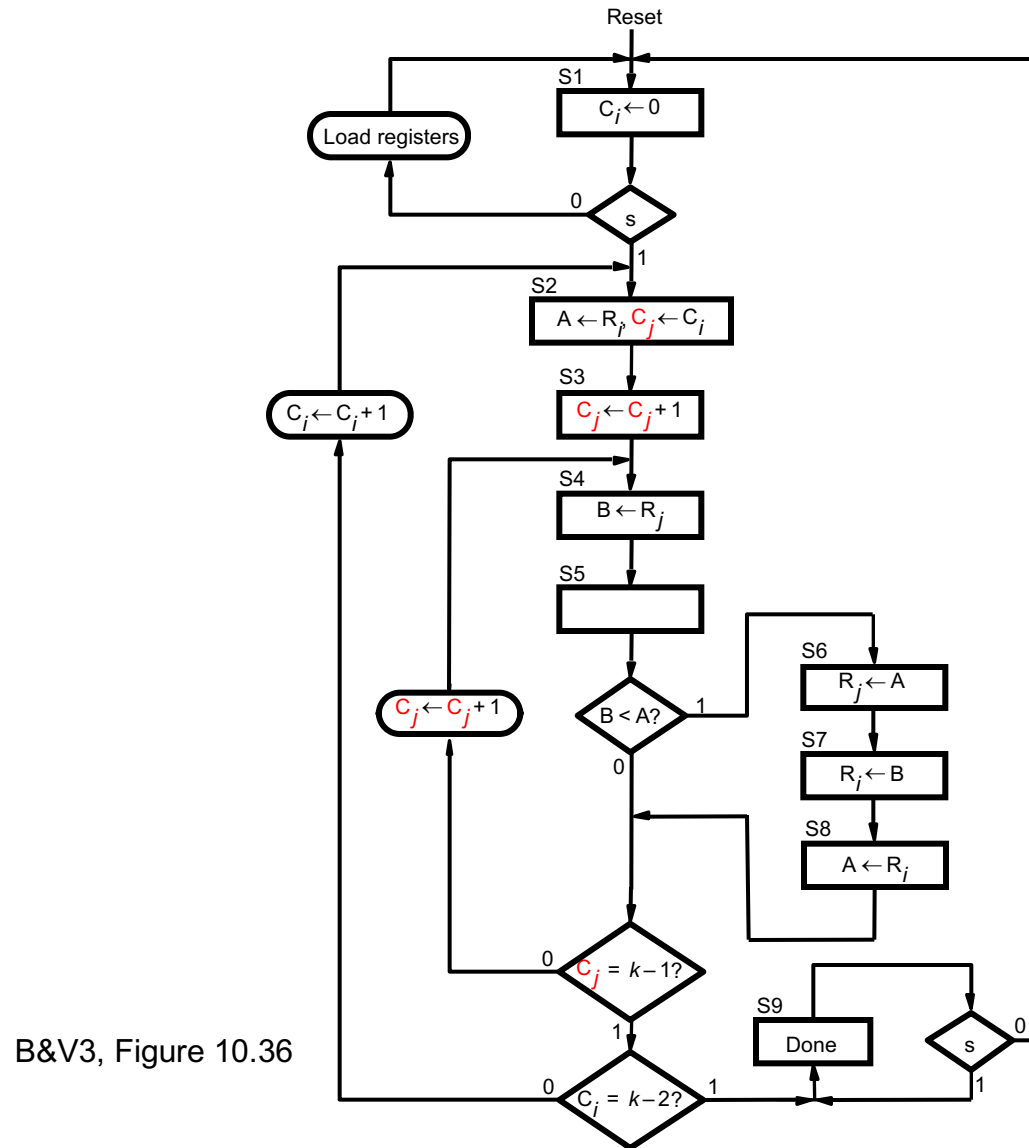


B&V3, Figure 10.36

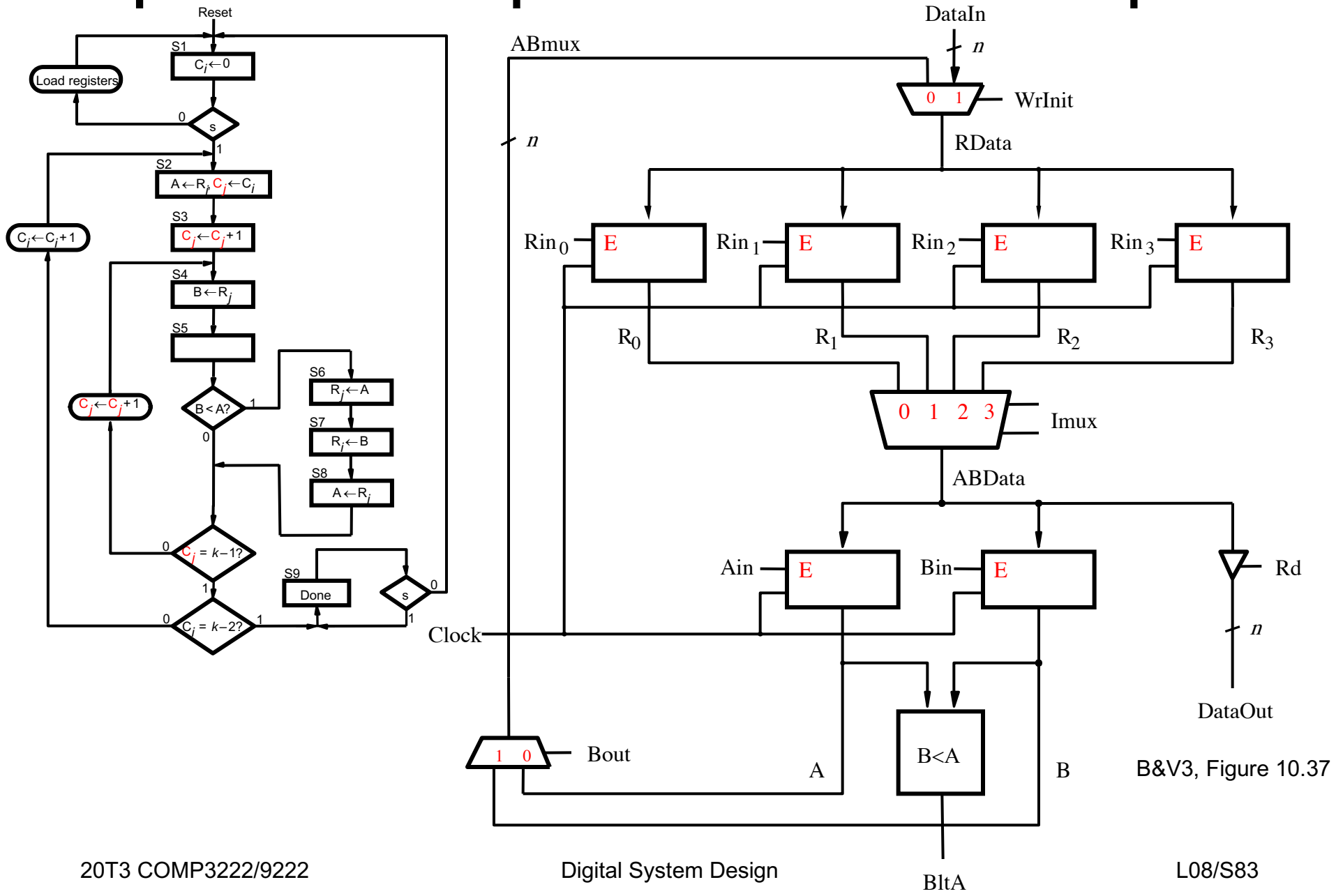A part of the datapath circuit for the sort op





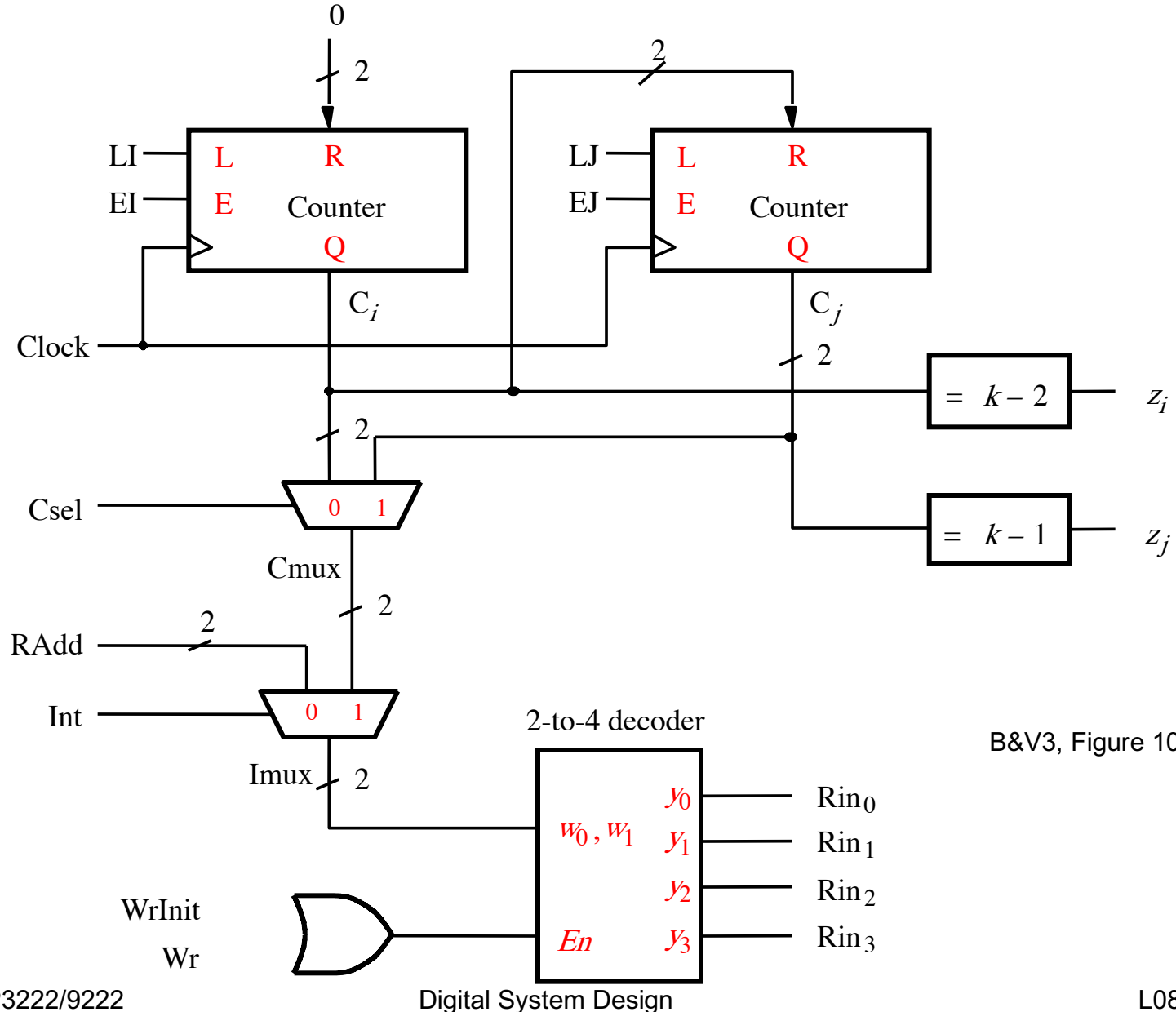A part of the datapath circuit for the sort op



ASM chart for the control circuit

B&V3, Figure 10.39

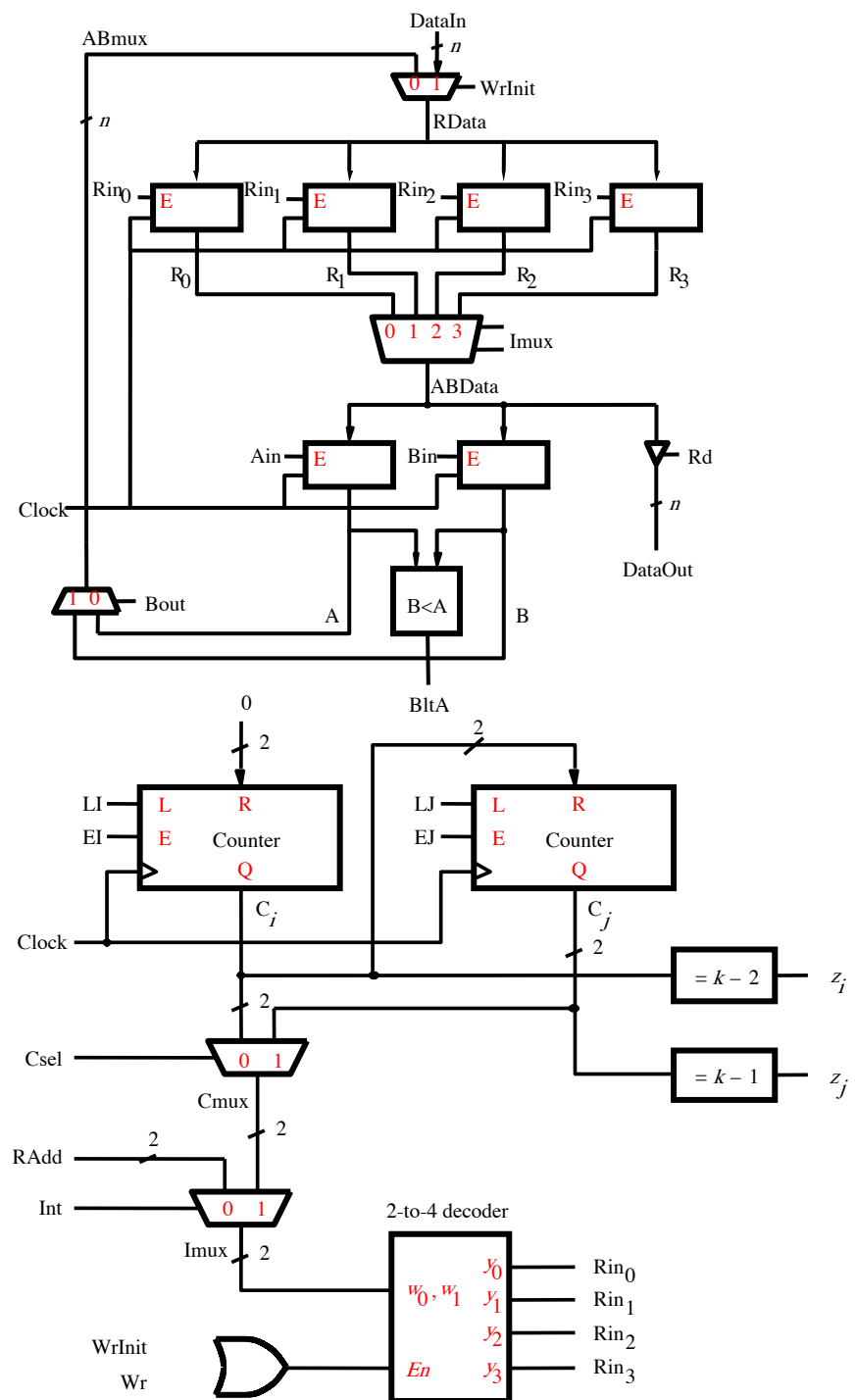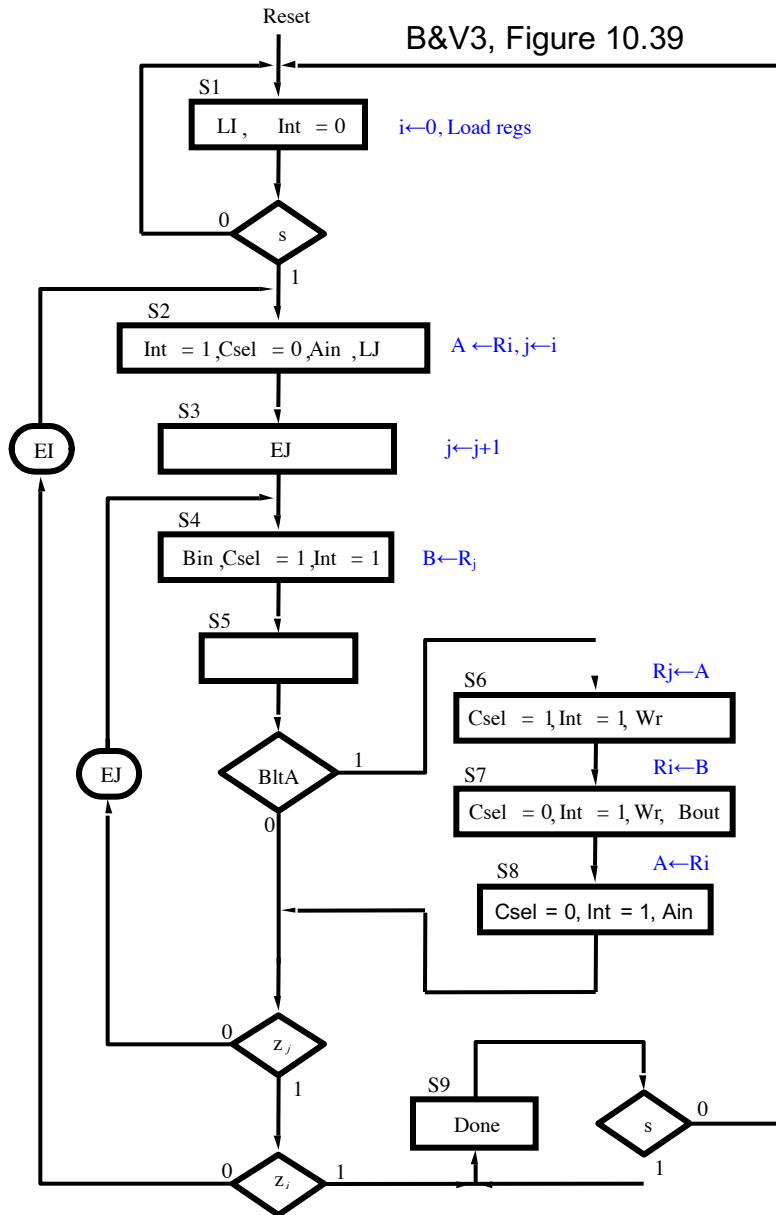

VHDL code for the sort operation (Part a)

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE work.components.all;
```


ENTITY sort IS

```
    GENERIC ( N : INTEGER := 4 );
    PORT ( Clock, Resetn : IN          STD_LOGIC ;
           s, WrInit, Rd  : IN          STD_LOGIC ;
           DataIn         : IN          STD_LOGIC_VECTOR(N-1 DOWNTO 0);
           RAdd           : IN          INTEGER RANGE 0 TO 3 ;
           DataOut        : BUFFER STD_LOGIC_VECTOR(N-1 DOWNTO 0);
           Done           : BUFFER STD_LOGIC );
```

END sort ;

ARCHITECTURE Behavior OF sort IS

```
    TYPE State_type IS ( S1, S2, S3, S4, S5, S6, S7, S8, S9 );
    SIGNAL y : State_type ;
    SIGNAL Ci, Cj : INTEGER RANGE 0 TO 3 ;
    SIGNAL Rin : STD_LOGIC_VECTOR(3 DOWNTO 0);
    TYPE RegArray IS
        ARRAY(3 DOWNTO 0) OF STD_LOGIC_VECTOR(N-1 DOWNTO 0);
    SIGNAL R : RegArray ;
    SIGNAL RData, ABMux : STD_LOGIC_VECTOR(N-1 DOWNTO 0);
    SIGNAL Int, Csel, Wr, BltA : STD_LOGIC ;
    SIGNAL CMux, IMux : INTEGER RANGE 0 TO 3 ;
    SIGNAL Ain, Bin, Bout : STD_LOGIC ;
    SIGNAL LI, LJ, EI, EJ, zi, zj : STD_LOGIC ;
    SIGNAL Zero : INTEGER RANGE 3 DOWNTO 0 ; -- parallel data for Ci = 0
    SIGNAL A, B, ABData : STD_LOGIC_VECTOR(N-1 DOWNTO 0);
```

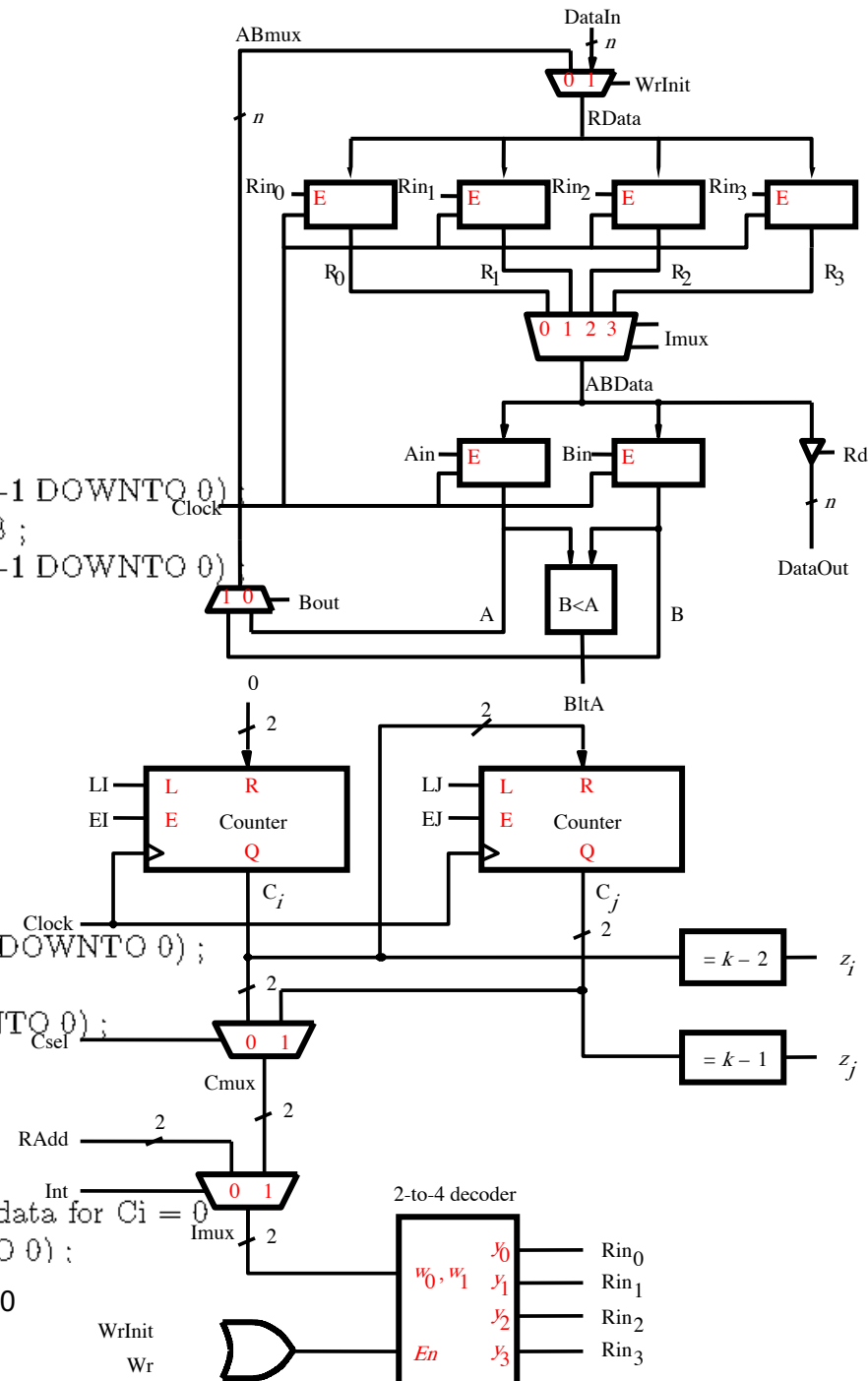

B&V3, Figure 10.40

VHDL code for the sort operation (Part *b*)

```


BEGIN
  FSM_transitions: PROCESS ( Resetn, Clock )
  BEGIN
    IF Resetn = '0' THEN
      y <= S1 ;
    ELSIF (Clock'EVENT AND Clock = '1') THEN
      CASE y IS
        WHEN S1 => IF S = '0' THEN y <= S1 ;
                    ELSE y <= S2 ; END IF ;
        WHEN S2 => y <= S3 ;
        WHEN S3 => y <= S4 ;
        WHEN S4 => y <= S5 ;
        WHEN S5 => IF BltA = '1' THEN y <= S6 ;
                    ELSE y <= S8 ; END IF ;
        WHEN S6 => y <= S7 ;
        WHEN S7 => y <= S8 ;
        WHEN S8 =>
          IF zj = '0' THEN y <= S4 ;
          ELSIF zi = '0' THEN y <= S2 ;
          ELSE y <= S9 ;
          END IF ;
        WHEN S9 => IF s = '1' THEN y <= S9 ; ELSE y <= S1 ; END IF ;
      END CASE ;
    END IF ;
  END PROCESS ;

```

B&V3, Figure 10.40

Note that the text executes S8 irrespective of need in order to simplify the control.

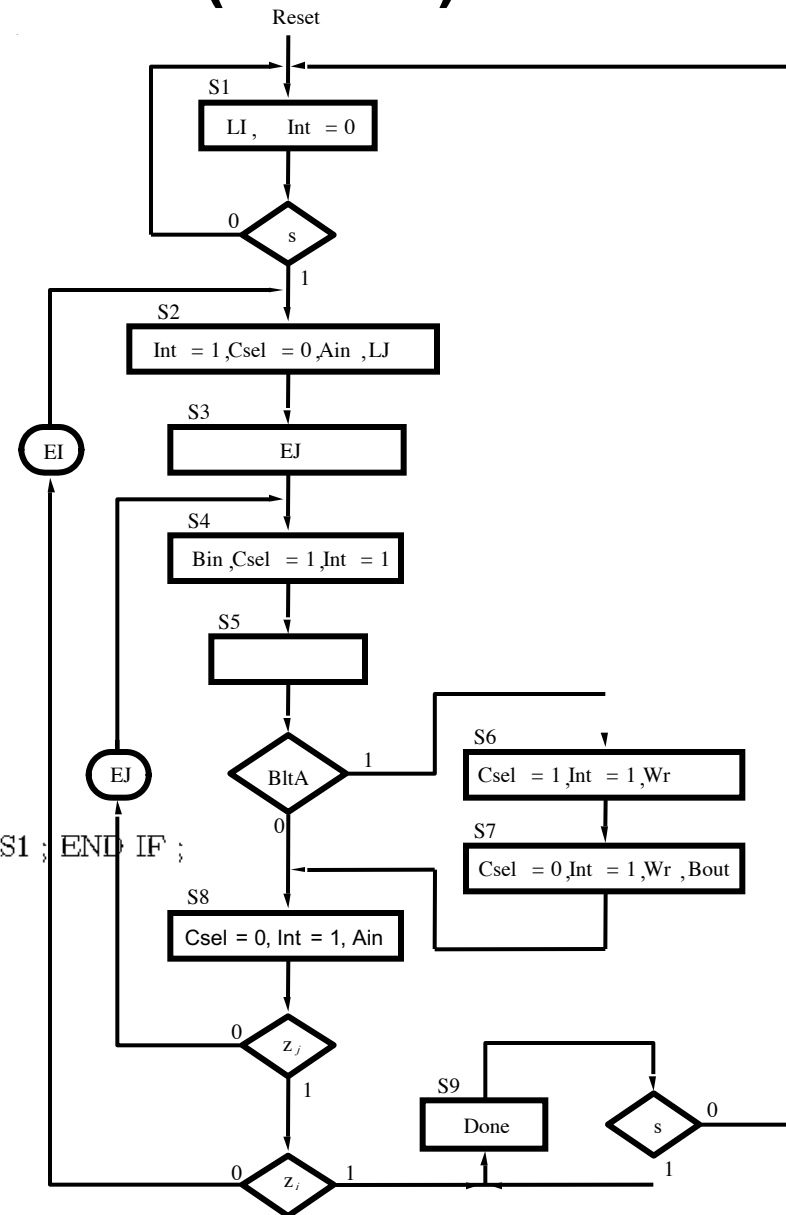
What are the costs/benefits of this approach?



VHDL code for the sort operation (Part c)

```
-- define the outputs generated by the FSM
Int <= '0' WHEN y = S1 ELSE '1';
Done <= '1' WHEN y = S9 ELSE '0';
FSM_outputs: PROCESS ( y, zi, zj )
BEGIN
    LI <= '0'; LJ <= '0'; EI <= '0'; EJ <= '0'; Csel <= '0';
    Wr <= '0'; Ain <= '0'; Bin <= '0'; Bout <= '0';
    CASE y IS
        WHEN S1 => LI <= '1';
        WHEN S2 => Ain <= '1'; LJ <= '1';
        WHEN S3 => EJ <= '1';
        WHEN S4 => Bin <= '1'; Csel <= '1';
        WHEN S5 => -- no outputs asserted in this state
        WHEN S6 => Csel <= '1'; Wr <= '1';
        WHEN S7 => Wr <= '1'; Bout <= '1';
        WHEN S8 => Ain <= '1';
        IF zj = '0' THEN
            EJ <= '1';
        ELSE
            EJ <= '0';
            IF zi = '0' THEN
                EI <= '1';
            ELSE
                EI <= '0';
            END IF;
        END IF;
        WHEN S9 => -- Done is assigned 1 by conditional signal assignment
    END CASE;
END PROCESS;
```

B&V3, Figure 10.40

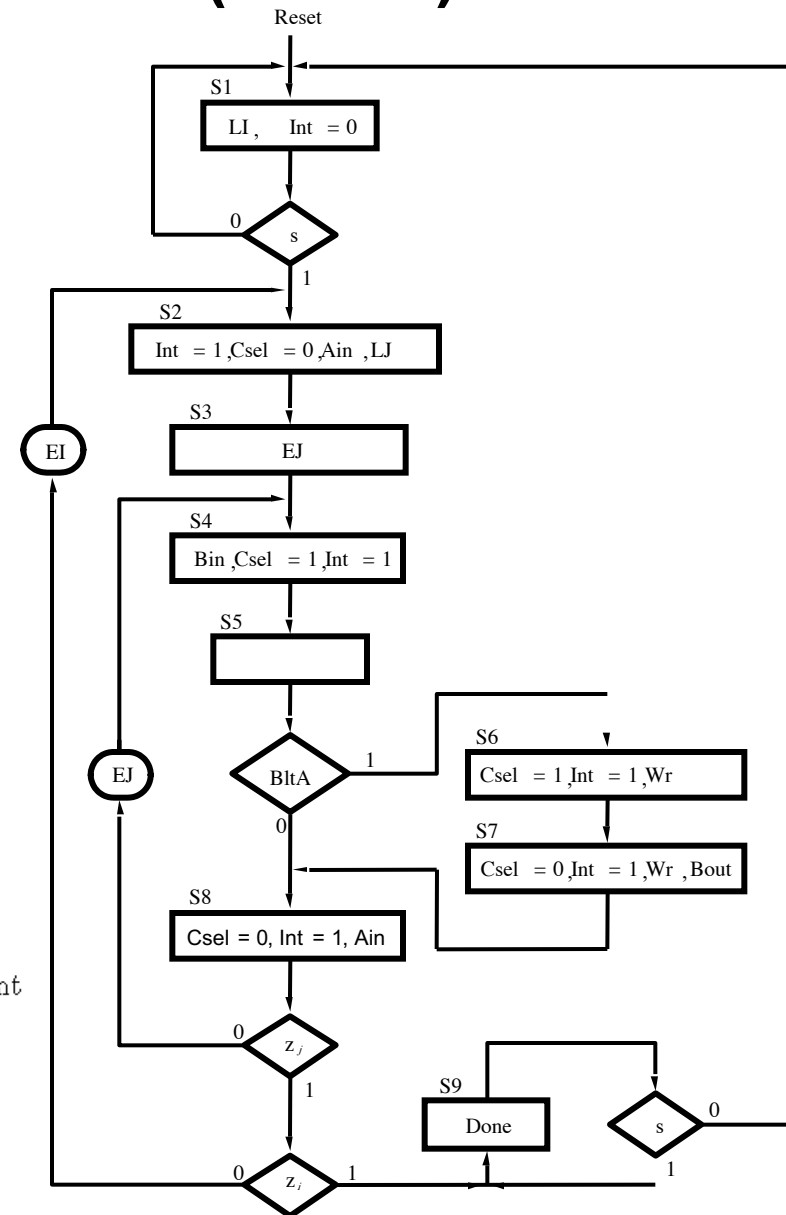

VHDL code for the sort operation (Part e)

```
RinDec: PROCESS ( WrInit, Wr, IMux )
BEGIN
```

```
  IF (WrInit OR Wr) = '1' THEN
```

```
    CASE IMux IS
```

```
      WHEN 0 => Rin <= "0001" ;
```

```
      WHEN 1 => Rin <= "0010" ;
```

```
      WHEN 2 => Rin <= "0100" ;
```

```
      WHEN OTHERS => Rin <= "1000" ;
```

```
    END CASE ;
```

```
  ELSE Rin <= "0000" ;
```

```
  END IF ;
```

```
END PROCESS ;
```

```
Zi <= '1' WHEN Ci = 2 ELSE '0' ;
```

```
Zj <= '1' WHEN Cj = 3 ELSE '0' ;
```

```
DataOut <= (OTHERS => 'Z') WHEN Rd = '0' ELSE ABData ;
```

```
END Behavior ;
```

B&V3, Figure 10.40

